
Digital System Design

Lecture 4

Modeling Combinational Circuits in VHDL

◦ **Reading Assignment:**

- Brown, “Fundamentals of Digital Logic with VHDL”, pp. 60 - 65, pp. 318 – 364
- Brown, “Appendix A: VHDL Reference”, pp. 791 - 811

◦ **Learning Objective:**

- Design a VHDL model for a combinational logic circuit using **concurrent** modeling techniques
 - signal assignments and logical operators
 - conditional signal assignments
 - selected signal assignments
- Design a VHDL model for a combinational logic circuit using **sequential** modeling techniques
- Design a VHDL model for a combinational logic circuit using a **structural** design approach

Concurrent Signal Assignments

- A simple concurrent signal assignments are accomplished by using the `<=` operator after the begin statement in the architecture.


`signal_name <= expression ;`

- Each individual assignment will be executed concurrently and synthesized as separate logic circuits.

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity con_vhdl is
port (A,B,C,D: in STD_LOGIC;
      E,F,G : out STD_LOGIC);
end con_vhdl;

 architecture a of con_vhdl is
begin
  E <= A and B;
  F <= not C;
  G <= not D;
end a;
```



Selected and Conditional Signal Assignments


- A **selected signal assignment** is used to set the value of a signal to one of several alternatives based on a selection criterion. The general form is

```
WITH expression SELECT
    signal_name <= expression WHEN constant_value{,
                                expression WHEN constant_value} ;
```


- Similar to the selected signal assignment, the **conditional signal assignment** is used to set a signal to one of several alternative values. The general form is

```
signal_name <= expression WHEN logic_expression ELSE
    {expression WHEN logic_expression ELSE}
expression ;
```

Multiplexers

 


A 2-to-1 multiplexer

 

(a) Graphical symbol


s	f
0	w_0
1	w_1

(b) Truth table

 

(c) Sum-of-products circuit


A 4-to-1 multiplexer

 

(a) Graphic symbol


s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table

 


(c) Circuit


Using 2-to-1 multiplexers to build a 4-to-1 multiplexer

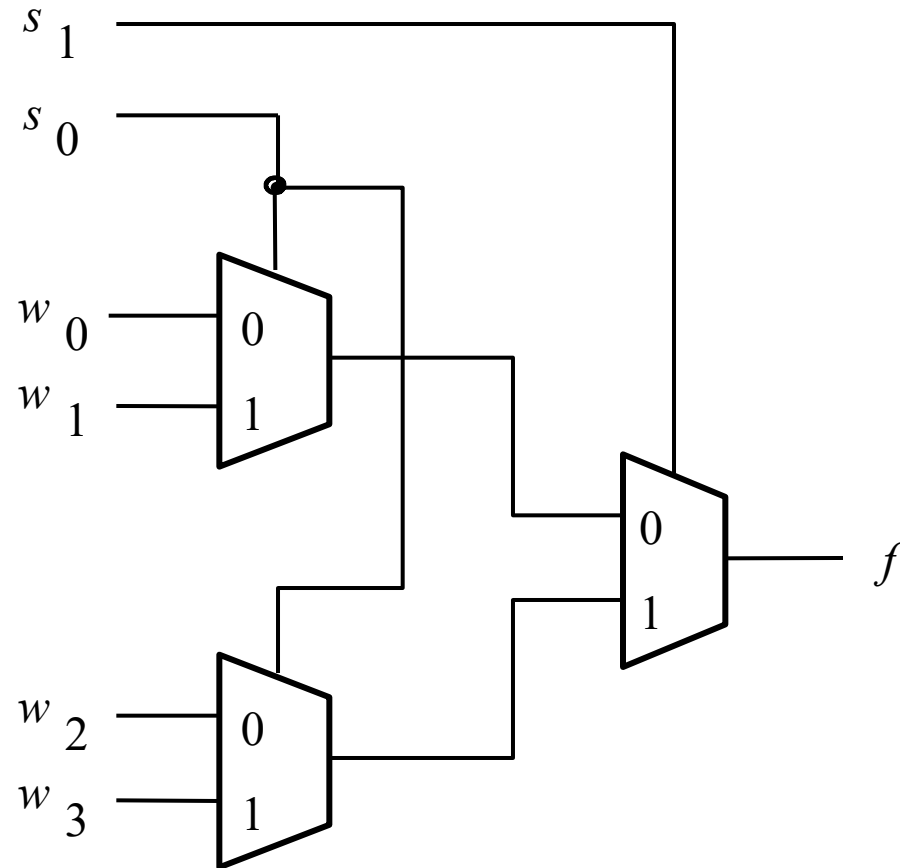

 
Using 4-to-1 multiplexers to build a 16-to-1 multiplexer



A practical application of multiplexers

 


(a) A 2x2 crossbar switch

 

 (b) Implementation using multiplexers

Multiplexer Function Realization

Determine the multiplexer data input values for realizing the function $F(X,Y,Z) = X \cdot Z + X' \cdot (Y \oplus Z)$




$$\begin{aligned} F(X,Y,Z) &= X \cdot Z + X' \cdot (Y \oplus Z) \\ &= X \cdot Z + X' \cdot (Y' \cdot Z + Y \cdot Z') \\ &= X \cdot Z + X' \cdot Y' \cdot Z + X' \cdot Y \cdot Z' \end{aligned}$$

X \ YZ	00	01	10	11
0	0	1	0	1
1	0	1	1	0

$$F(X,Y,Z) = \sum_{X,Y,Z}(1,2,5,7)$$

Synthesis of a logic function using multiplexers

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

 


(a) Implementation using a 4-to-1 multiplexer

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

w_1	f
0	w_2
1	$\overline{w_2}$

(b) Modified truth table

 

(c) Circuit

VHDL code for a 2-to-1 multiplexer

Use selected signal assignment

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s      : IN      STD_LOGIC ;
           f              : OUT     STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    WITH s SELECT
        f <= w0 WHEN '0',
           w1 WHEN OTHERS ;
END Behavior ;
```

VHDL code for a 4-to-1 multiplexer

Use selected signal assignment

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux4to1 IS
    PORT ( w0, w1, w2, w3    : IN      STD_LOGIC ;
           s                  : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           f                  : OUT     STD_LOGIC ) ;
END mux4to1 ;

ARCHITECTURE Behavior OF mux4to1 IS
BEGIN
    WITH s SELECT
        f <= w0 WHEN "00",
            w1 WHEN "01",
            w2 WHEN "10",
            w3 WHEN OTHERS ;
END Behavior ;
```

Alternate VHDL code for a 2-to-1 multiplexer

Use conditional signal assignment

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s      : IN      STD_LOGIC ;
           f              : OUT     STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    f <= w0 WHEN s = '0' ELSE w1 ;
END Behavior ;
```

Alternate VHDL code for a 4-to-1 multiplexer

Use conditional signal assignment

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux4to1 IS
    PORT ( w0, w1, w2, w3      : IN      STD_LOGIC ;
           s                  : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           f                  : OUT     STD_LOGIC ) ;
END mux4to1 ;

ARCHITECTURE Behavior OF mux4to1 IS
BEGIN
    f <= w0 WHEN s = "00" ELSE
        w1 WHEN s = "01" ELSE
        w2 WHEN s = "10" ELSE
        w3;
END Behavior ;
```


VHDL code for a 16-to-1 multiplexer


```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY mux16to1 IS  
    PORT (    w    : IN        STD_LOGIC_VECTOR(0 TO 15) ;  
            s    : IN        STD_LOGIC_VECTOR(3 DOWNT0 0) ;  
            f    : OUT       STD_LOGIC ) ;  
END mux16to1 ;
```

```
ARCHITECTURE Structure OF mux16to1 IS  
    SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;  
    COMPONENT mux4to1  
        PORT (    w0, w1, w2, w3 : IN        STD_LOGIC ;  
                s                : IN        STD_LOGIC_VECTOR(1 DOWNT0 0) ;  
                f                : OUT       STD_LOGIC ) ;  
    END COMPONENT ;
```

```
BEGIN  
    Mux1: mux4to1 PORT MAP ( w(0), w(1), w(2), w(3), s(1 DOWNT0 0), m(0) ) ;  
    Mux2: mux4to1 PORT MAP ( w(4), w(5), w(6), w(7), s(1 DOWNT0 0), m(1) ) ;  
    Mux3: mux4to1 PORT MAP ( w(8), w(9), w(10), w(11), s(1 DOWNT0 0), m(2) ) ;  
    Mux4: mux4to1 PORT MAP ( w(12), w(13), w(14), w(15), s(1 DOWNT0 0), m(3) ) ;  
    Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2), m(3), s(3 DOWNT0 2), f ) ;  
END Structure ;
```


Decoders/Encoders

 


A 2-to-4 decoder

En	I_1	I_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 


(b) Graphic symbol

 


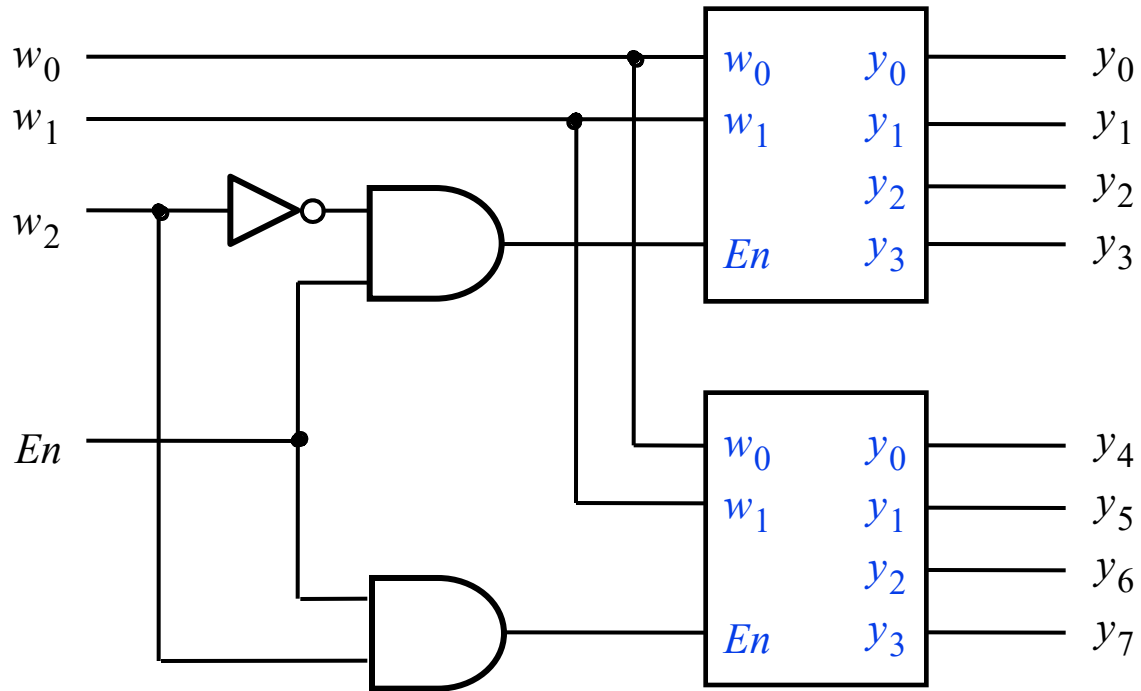(c) Logic circuit

A 3-to-8 decoder using two 2-to-4 decoders



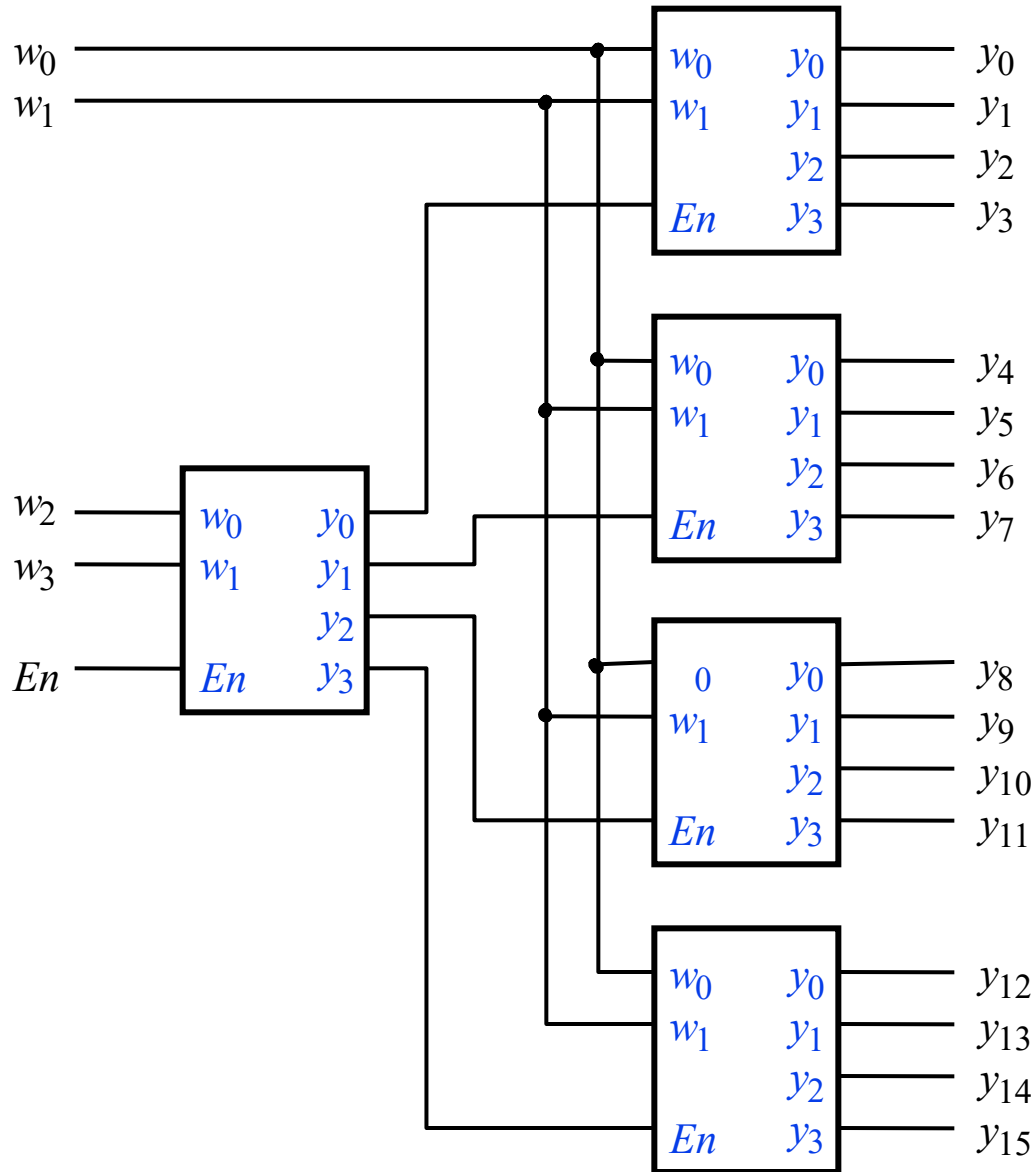A 4-to-16 decoder built using a decoder tree



VHDL code for a 2-to-4 binary decoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec2to4 IS
    PORT ( w   : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           En  : IN      STD_LOGIC ;
           y   : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
END dec2to4 ;

ARCHITECTURE Behavior OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y <= "1000" WHEN "100",
            "0100" WHEN "101",
            "0010" WHEN "110",
            "0001" WHEN "111",
            "0000" WHEN OTHERS ;
END Behavior ;
```


Alternate VHDL code for a 2-to-4 binary decoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec2to4 IS
    PORT ( w   : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           En  : IN      STD_LOGIC ;
           y   : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
END dec2to4 ;


ARCHITECTURE Behavior OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
BEGIN
    Enw <= En & w ;
    y <= "1000" WHEN Enw = "100" ELSE
        "0100" WHEN Enw = "101" ELSE
        "0010" WHEN Enw = "110" ELSE
        "0001" WHEN Enw = "111" ELSE
        "0000" ;
END Behavior ;
```

A 4-to-2 binary encoder

 

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1


(a) Truth table

 

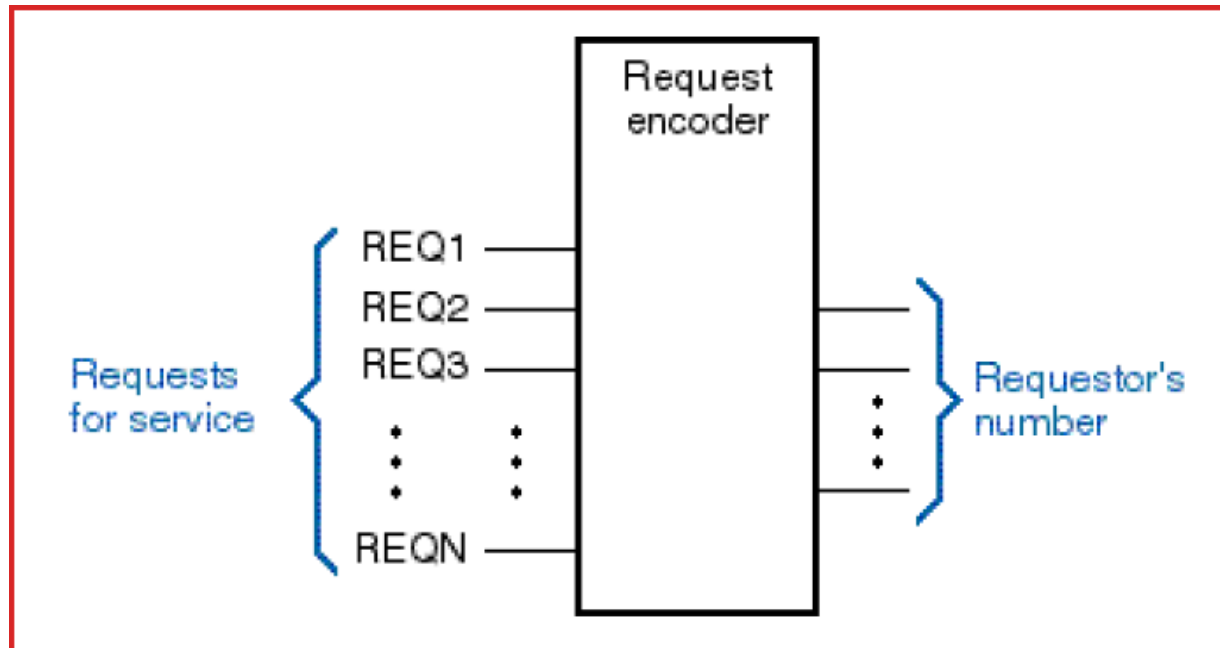(b) Circuit

Priority Encoders

- A common application is to encode the number of a device requesting service from a microprocessor-based system



Problem: More than one device may be requesting service at any given time

Priority Encoders

- Solution: Assign *priority* to the input lines, such that when multiple inputs are asserted simultaneously, the *highest priority* (i.e. *highest numbered*) input “wins” – such a device is called a *priority encoder*

Truth table for a 4-to-2 priority encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \overline{w_3}\overline{w_2}\overline{w_1}w_0$$

$$i_1 = \overline{w_3}\overline{w_2}w_1$$

$$i_2 = \overline{w_3}w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

Less Efficient code for a priority encoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority IS
    PORT ( w : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
           y : OUT     STD_LOGIC_VECTOR(1 DOWNT0 0) ;
           z : OUT     STD_LOGIC ) ;
END priority ;

ARCHITECTURE Behavior OF priority IS
BEGIN
    WITH w SELECT
        y <=  "00" WHEN "0001",
              "01" WHEN "0010",
              "01" WHEN "0011",
              "10" WHEN "0100",
              "10" WHEN "0101",
              "10" WHEN "0110",
              "10" WHEN "0111",
              "11" WHEN OTHERS ;

    WITH w SELECT
        z <=  '0' WHEN "0000",
              '1' WHEN OTHERS ;
END Behavior ;
```


Better VHDL code for a priority encoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;


ENTITY priority IS
    PORT ( w    : IN    STD_LOGIC_VECTOR(3 DOWNT0 0) ;
           y    : OUT   STD_LOGIC_VECTOR(1 DOWNT0 0) ;
           z    : OUT   STD_LOGIC ) ;
END priority ;

ARCHITECTURE Behavior OF priority IS
BEGIN
    y <=  "11" WHEN w(3) = '1' ELSE
          "10" WHEN w(2) = '1' ELSE
          "01" WHEN w(1) = '1' ELSE
          "00" ;
    z <= '0' WHEN w = "0000" ELSE '1' ;
END Behavior ;
```


Other Combinational Circuits

 

 A BCD-to-7-segment display code converter



(a) Code converter

 


(b) 7-segment display

w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

(c) Truth table

Comparison Circuits

 

VHDL code for a 4-bit comparator

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY compare IS
    PORT ( A, B          : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
          AeqB, AgtB, AltB : OUT    STD_LOGIC ) ;
END compare ;

ARCHITECTURE Behavior OF compare IS
BEGIN
    AeqB <= '1' WHEN A = B ELSE '0' ;
    AgtB <= '1' WHEN A > B ELSE '0' ;
    AltB <= '1' WHEN A < B ELSE '0' ;
END Behavior ;
```

 

VHDL code for a 4-bit comparator

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_arith.all ;

ENTITY compare IS
    PORT ( A, B          : IN      SIGNED(3 DOWNT0 0) ;
          AeqB, AgtB, AltB : OUT    STD_LOGIC ) ;
END compare ;

ARCHITECTURE Behavior OF compare IS
BEGIN
    AeqB <= '1' WHEN A = B ELSE '0' ;
    AgtB <= '1' WHEN A > B ELSE '0' ;
    AltB <= '1' WHEN A < B ELSE '0' ;
END Behavior ;
```

Process Statements



Concurrent vs. Sequential

- All previous statements are called *concurrent assignment statements* because order does not matter.
- When order matters, the statements are called *sequential assignment statements*.
- All sequential assignment statements are placed within a *process statement*.

Process Statement

- Begins with PROCESS keyword followed by a *process (XX)* **sensitivity list**. *当 Process 之值改变时, 底下的 assignment 才会生效*
- For a combinational circuit, sensitivity list includes all input signals used in the process.
- Process executed whenever there is a change on a signal in the sensitivity list.
- Statements executed in sequential order.
- No assignments are visible until all statements in the process have been executed.
- If multiple assignments, only last has an effect.

A 2-to-1 multiplexer specified using **if-then-else**

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s      : IN      STD_LOGIC ;
           f              : OUT     STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        IF s = '0' THEN
            f <= w0 ;
        ELSE
            f <= w1 ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Alternative code for a 2-to-1 multiplexer

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s      : IN      STD_LOGIC ;
           f              : OUT     STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        f <= w0 ;
        IF s = '1' THEN
            f <= w1 ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

要s改变才会改变f的值 (w0 → w1, w1 → w0) → 形成multiplexer
↳ 記憶性

VHDL code with implied Memory

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY implied IS
    PORT (    A, B      : IN      STD_LOGIC ;
            AeqB       : OUT     STD_LOGIC ) ;
END implied ;

ARCHITECTURE Behavior OF implied IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        IF A = B THEN
            AeqB <= '1' ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

A priority encoder specified using **if-then-else**

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY priority IS
    PORT (    w    : IN        STD_LOGIC_VECTOR(3 DOWNT0 0) ;
            y    : OUT        STD_LOGIC_VECTOR(1 DOWNT0 0) ;
            z    : OUT        STD_LOGIC ) ;
END priority ;

ARCHITECTURE Behavior OF priority IS
BEGIN
    PROCESS ( w )
    BEGIN
        IF w(3) = '1' THEN
            y <= "11" ;
        ELSIF w(2) = '1' THEN
            y <= "10" ;
        ELSIF w(1) = '1' THEN
            y <= "01" ;
        ELSE
            y <= "00" ;
        END IF ;
    END PROCESS ;
    z <= '0' WHEN w = "0000" ELSE '1' ;
END Behavior ;
```


Alternative code for the priority encoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority IS
    PORT (    w    : IN        STD_LOGIC_VECTOR(3 DOWNTO 0) ;
            y    : OUT        STD_LOGIC_VECTOR(1 DOWNTO 0) ;
            z    : OUT        STD_LOGIC ) ;
END priority ;

ARCHITECTURE Behavior OF priority IS
BEGIN
    PROCESS ( w )
    BEGIN
        y <= "00" ;
        IF w(1) = '1' THEN y <= "01" ; END IF ;
        IF w(2) = '1' THEN y <= "10" ; END IF ;
        IF w(3) = '1' THEN y <= "11" ; END IF ;

        z <= '1' ;
        IF w = "0000" THEN z <= '0' ; END IF ;
    END PROCESS ;
END Behavior ;
```

A 2-to-1 multiplexer specified using a CASE statement

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT (    w0, w1, s    : IN    STD_LOGIC ;
            f              : OUT   STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        CASE s IS
            WHEN '0' =>
                f <= w0 ;
            WHEN OTHERS =>
                f <= w1 ;
        END CASE ;
    END PROCESS ;
END Behavior ;
```

A 2-to-4 binary decoder specified using a **CASE** statement

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY dec2to4 IS
    PORT (    w    : IN        STD_LOGIC_VECTOR(1 DOWNTO 0) ;
            En    : IN        STD_LOGIC ;
            y      : OUT       STD_LOGIC_VECTOR(0 TO 3) ) ;
END dec2to4 ;

ARCHITECTURE Behavior OF dec2to4 IS
BEGIN
    PROCESS ( w, En )
    BEGIN
        IF En = '1' THEN
            CASE w IS
                WHEN "00" =>    y <= "1000" ;
                WHEN "01" =>    y <= "0100" ;
                WHEN "10" =>    y <= "0010" ;
                WHEN OTHERS =>  y <= "0001" ;
            END CASE ;
        ELSE
            y <= "0000" ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

A BCD-to-7-segment decoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY seg7 IS
    PORT (    bcd      : IN          STD_LOGIC_VECTOR(3 DOWNTO 0) ;
            leds       : OUT          STD_LOGIC_VECTOR(1 TO 7) ) ;
END seg7 ;
ARCHITECTURE Behavior OF seg7 IS
BEGIN
    PROCESS ( bcd )
    BEGIN
        CASE bcd IS --
            WHEN "0000"    => leds <= "1111110" ;
            WHEN "0001"    => leds <= "0110000" ;
            WHEN "0010"    => leds <= "1101101" ;
            WHEN "0011"    => leds <= "1111001" ;
            WHEN "0100"    => leds <= "0110011" ;
            WHEN "0101"    => leds <= "1011011" ;
            WHEN "0110"    => leds <= "1011111" ;
            WHEN "0111"    => leds <= "1110000" ;
            WHEN "1000"    => leds <= "1111111" ;
            WHEN "1001"    => leds <= "1110011" ;
            WHEN OTHERS    => leds <= "-----" ;
        END CASE ;
    END PROCESS ;
END Behavior ;
```

The functionality of the 74381 ALU

Operation	Inputs	Outputs
	s_2 s_1 s_0	F
Clear	0 0 0	0 0 0 0
B−A	0 0 1	$B - A$
A−B	0 1 0	$A - B$
ADD	0 1 1	$A + B$
XOR	1 0 0	$A \text{ XOR } B$
OR	1 0 1	$A \text{ OR } B$
AND	1 1 0	$A \text{ AND } B$
Preset	1 1 1	1 1 1 1

Code that represents the functionality of the 74381 ALU

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
ENTITY alu IS
    PORT ( s      : IN      STD_LOGIC_VECTOR(2 DOWNTO 0) ;
          A, B    : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          F       : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END alu ;

ARCHITECTURE Behavior OF alu IS
BEGIN
    PROCESS ( s, A, B )
    BEGIN
        CASE s IS
            WHEN "000" => F <= "0000" ;
            WHEN "001" => F <= B - A ;
            WHEN "010" => F <= A - B ;
            WHEN "011" => F <= A + B ;
            WHEN "100" => F <= A XOR B ;
            WHEN "101" => F <= A OR B ;
            WHEN "110" => F <= A AND B ;
            WHEN OTHERS =>
                F <= "1111" ;
        END CASE ;
    END PROCESS ;
END Behavior ;
```