
Digital System Design


Lecture 8

Design Examples I

Learning Examples:


- **Frequency Generator**
 - 24時制電子鐘
- **Debounce Circuit**
- **LED control**
- **8x8 LED Matrix Control**

Frequency Generator

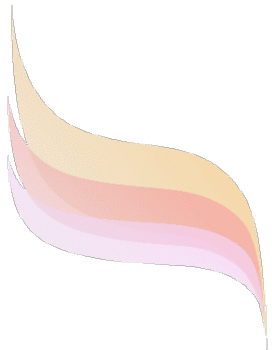

Frequency generator I


◆ 50Mhz to 1khz, 100hz, 10z, and 1hz

 

```
entity CLK_DIV is
  port
  (
    clock_50Mhz      : IN  STD_LOGIC;
    clock_1KHz       : OUT STD_LOGIC;
    clock_100Hz      : OUT STD_LOGIC;
    clock_10Hz       : OUT STD_LOGIC;
    clock_1Hz        : OUT STD_LOGIC);
end CLK_DIV;
```


Frequency generator II

◆ User-specified

 

```
entity CLK_GEN is
  generic( divisor: integer := 50_000_000 );
  port
  (
    clock_in      : IN  STD_LOGIC;
    clock_out     : OUT STD_LOGIC);
end CLK_GEN;
```

可顯示“時”：“分”：“秒”的24時制電子鐘

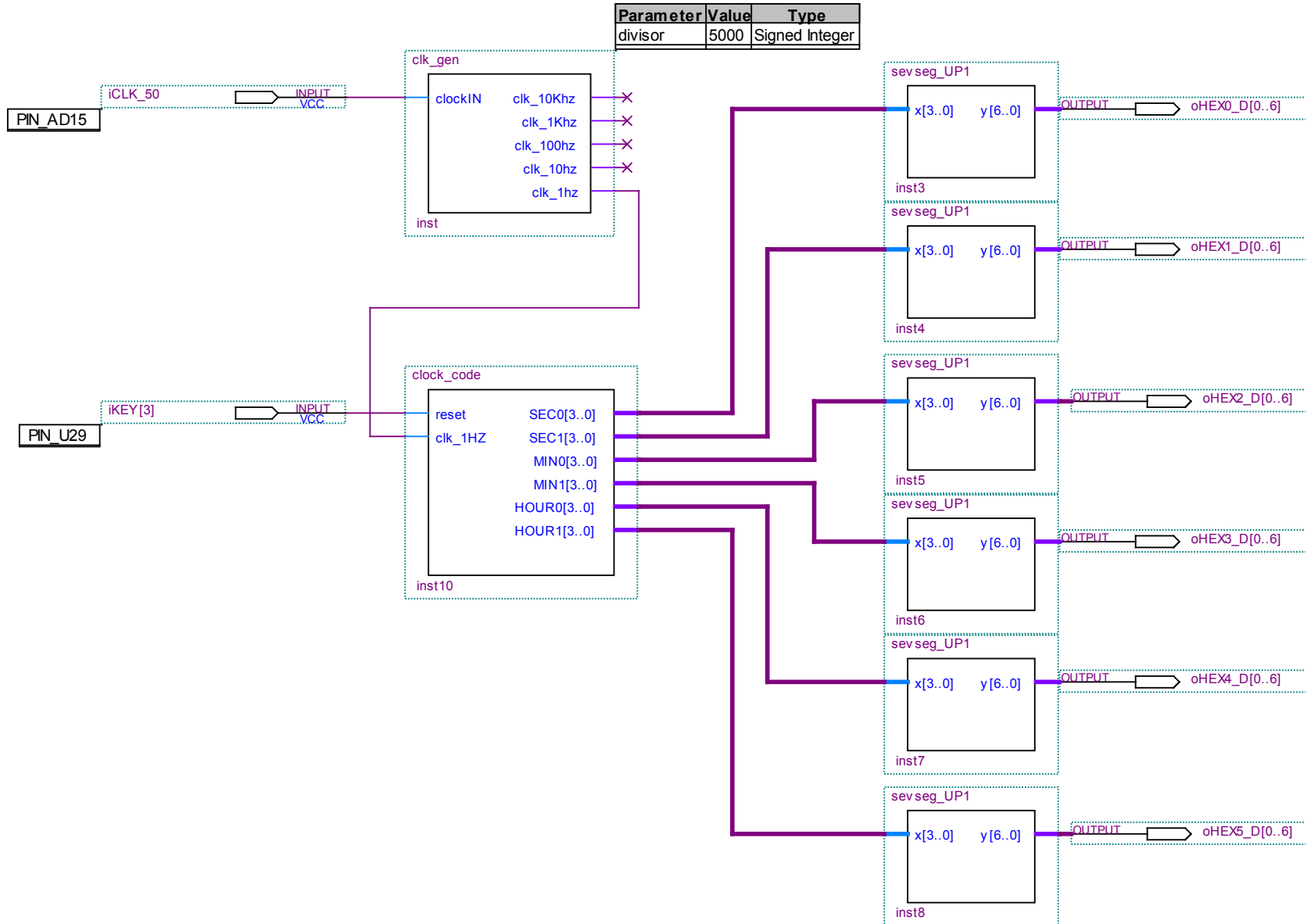

VHDL code

**ARCHITECTURE a OF clock_code IS
BEGIN**

**PROCESS (Clk_1HZ, reset)
BEGIN**

IF reset = '0' THEN

HOUR1<= X"0"; HOUR0<= X"0";

MIN1 <= X"0"; MIN0 <= X"0";

SEC1 <= X"0"; SEC0 <= X"0";

ELSIF clk_1HZ'EVENT AND clk_1HZ = '1' THEN

-- 個位數“秒”

IF SEC0 < 9 THEN

SEC0 <= SEC0 + 1;

ELSE

-- 十位數“秒”

SEC0 <= "0000";

IF SEC1 < 5 THEN

SEC1 <= SEC1 + 1;

ELSE

-- 個位數“分”

SEC1 <= "0000";

IF MIN0 < 9 THEN

MIN0 <= MIN0 + 1;

ELSE


-- 十位數“分”

MIN0 <= "0000";

IF MIN1 < 5 THEN

MIN1 <= MIN1 + 1;

ELSE

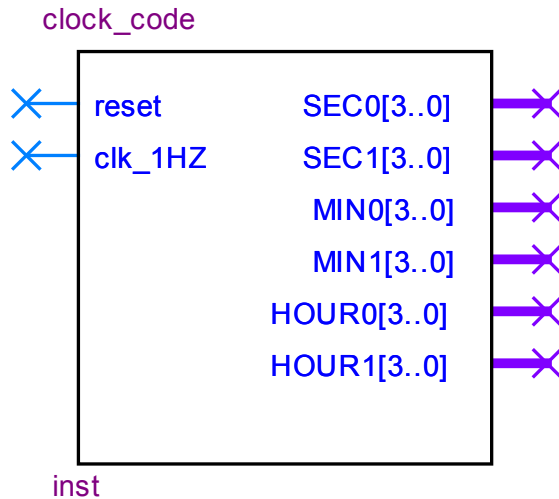

VHDL code

```
-- 個位數“時”
    MIN1 <= "0000";
    IF HOUR0 < 9 AND NOT((HOUR1=2) AND (HOUR0=3)) THEN
        HOUR0 <= HOUR0 + 1;
    ELSE
--十位數“時”
        IF NOT((HOUR1 = 2) AND (HOUR0 = 3)) THEN
            HOUR1 <= HOUR1 + 1;
            HOUR0 <= "0000";
        ELSE
-- 新的一天
            HOUR1 <= "0000";
            HOUR0 <= "0000";
        END IF;
    END IF;
END IF;
END IF;
END IF;
END IF;
END IF;
END IF;
END PROCESS;
END a;
```


LED Control



LED 單燈右移

□ 功能說明：

使用 CPLD 晶片，設計一個 LED 單燈右移的數位電路。LED 變化如圖 8-2 所示每秒單燈右移一次。

 


圖8-2 LED 單燈右移的變化情形

LED 單燈右移 (ror1bit.vhd)

□ 電路方塊圖：

如圖 8-3 所示為 LED 單燈右移電路方塊圖，包含除頻電路、LED 右移電路、反相電路等三個部份。

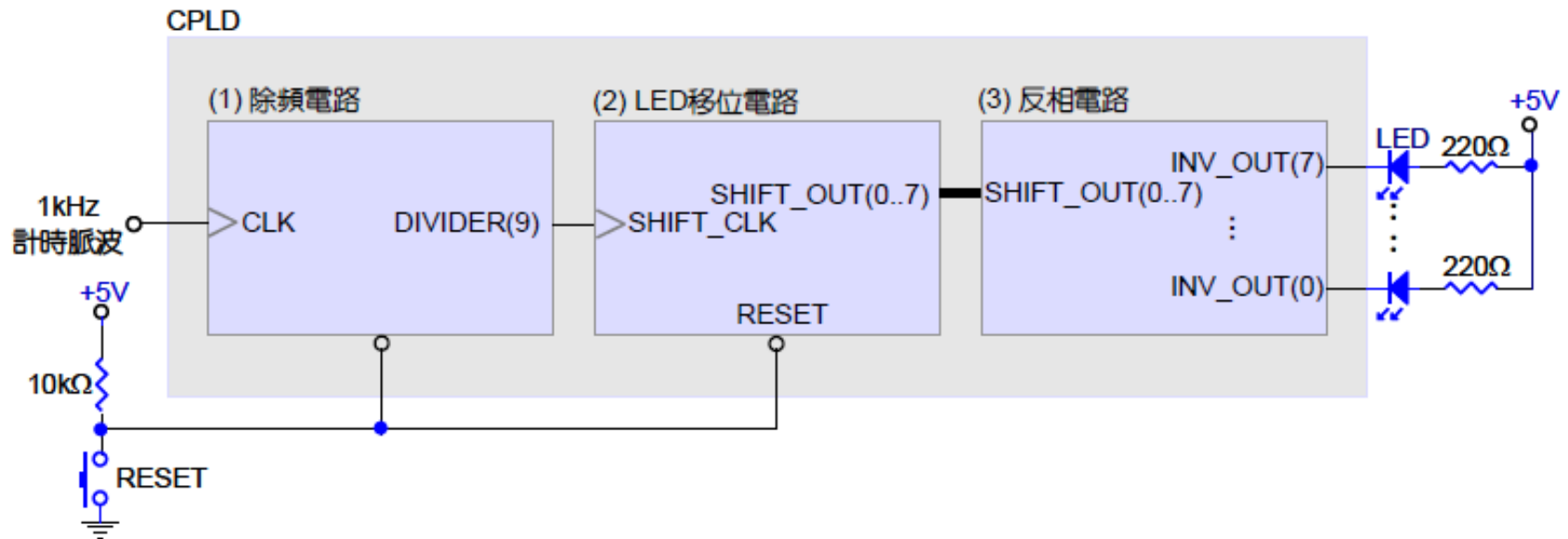


圖8-3 LED 單燈右移電路方塊圖

```

````library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

ENTITY lab71 IS
PORT (
 CLOCK_50 : IN STD_LOGIC; -- 輸入時脈
 KEY : IN STD_LOGIC_VECTOR(1 DOWNTO 0); -- 按鈕，使用 KEY[1] 作為重設
 LEDG : OUT STD_LOGIC_VECTOR(7 DOWNTO 0) -- LED 輸出
 --HEX0 : OUT STD_LOGIC_VECTOR(0 TO 6) -- 七段顯示器輸出
);
END lab71;

ARCHITECTURE Behavioral OF lab71 IS
 SIGNAL clk_div : INTEGER RANGE 0 TO 499999999 := 0; -- 用於生成 1Hz 的計時器
 SIGNAL led_counter : INTEGER RANGE 0 TO 7 := 0; -- LED 計數器
BEGIN
 PROCESS (CLOCK_50, KEY)
 BEGIN
 IF KEY(1) = '0' THEN -- 當按鈕按下（有效低）時重設
 led_counter <= 7; -- LED 計數器重置為 7
 LEDG <= "10000000"; -- 重置 LED 點亮狀態為 LEDG(7)
 clk_div <= 0; -- 計時器重置
 ELSIF rising_edge(CLOCK_50) THEN -- 在時脈的上升沿
 clk_div <= clk_div + 1; -- 計時器加 1

 IF clk_div = 499999999 THEN -- 每 50MHz 時脈下 250000000 次，即 1Hz
 clk_div <= 0; -- 重置計時器

 -- 使 led_counter 倒數
 IF led_counter = 0 THEN -- 當計數器為 0 時重置到 7
 led_counter <= 7;
 ELSE
 led_counter <= led_counter - 1; -- 否則減 1
 END IF;

 LEDG <= (others => '0'); -- 先將所有 LED 熄滅
 LEDG(led_counter) <= '1'; -- 點亮當前計數的 LED
 END IF;
 END IF;
 END PROCESS;
END Behavioral;
````

```

LED 單燈左右移 (霹靂燈)

□ 功能說明：

使用 CPLD 晶片，設計一個 LED 單燈左右移的數位電路。LED 如圖 8-6 所示，每 0.5 秒單燈左右來回移動。

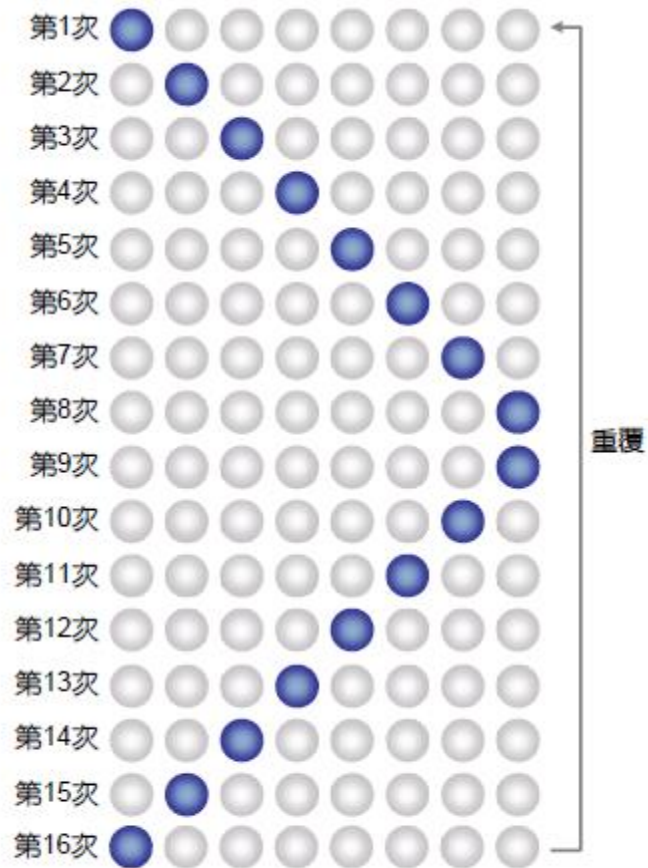


圖8-6 LED 單燈左右移的變化情形

LED 單燈左右移(霹靂燈) (pili1bit.vhd)

□ 電路方塊圖：

如圖 8-7 所示為 LED 單燈左右移電路方塊圖，包含除頻電路、除 16 計數電路、解碼電路等三個部份。

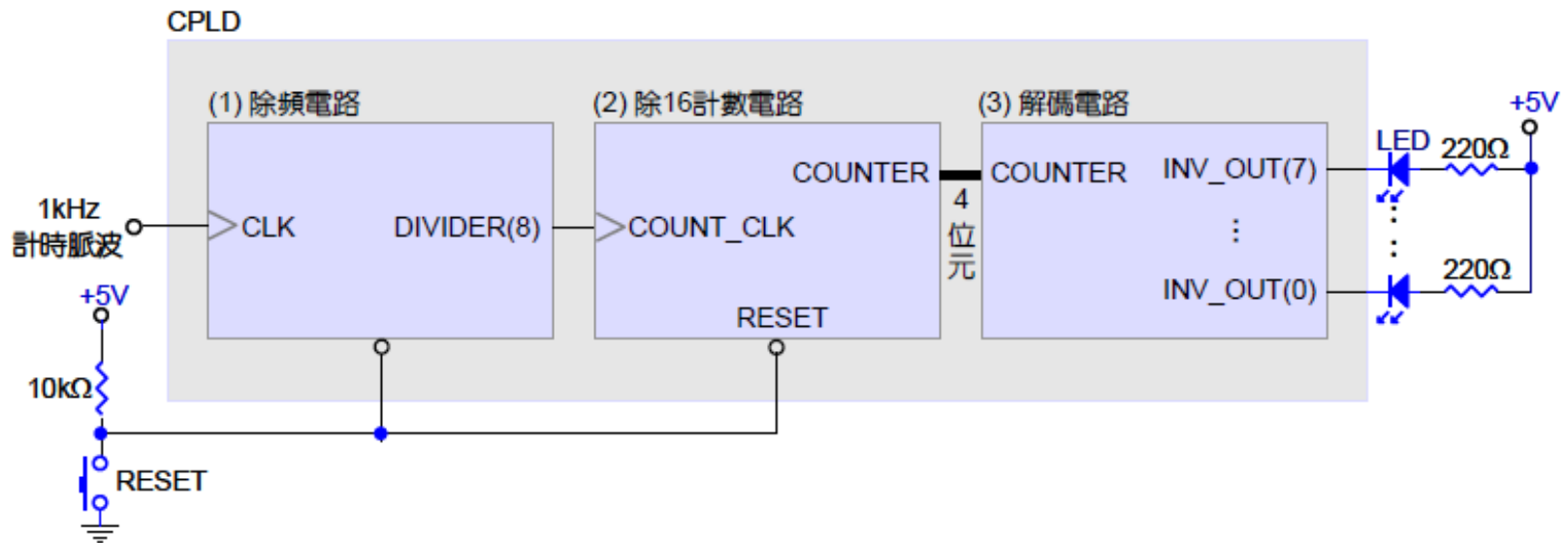


圖8-7 LED 單燈左右移電路方塊圖

指撥開關控制LED移位速度

□ 功能說明：

使用 CPLD 晶片，設計指撥開關控制 LED 單燈移位速度的數位電路。當指撥開關 S1 切至 ON 位置時，移位脈波為 1Hz，LED 移位速度最慢；當指撥開關 S2 切至 ON 位置時，移位脈波為 2Hz；當指撥開關 S3 切至 ON 位置時，移位脈波為 4Hz…餘依此類推；當指撥開關 S8 切至 ON 位置時，移位脈波為 128Hz，LED 移位速度最快。

☆令其中一個按鍵的優先級最高

Maybe 按 2 个以上令其不亮

指撥開關控制LED移位速度 (dip8_var_shift.vhd)

□ 電路方塊圖：

如圖 9-10 所示為指撥開關控制 LED 移位速度電路方塊圖，包含除頻電路、多工電路、LED 移位電路、緩衝電路等四個部份。

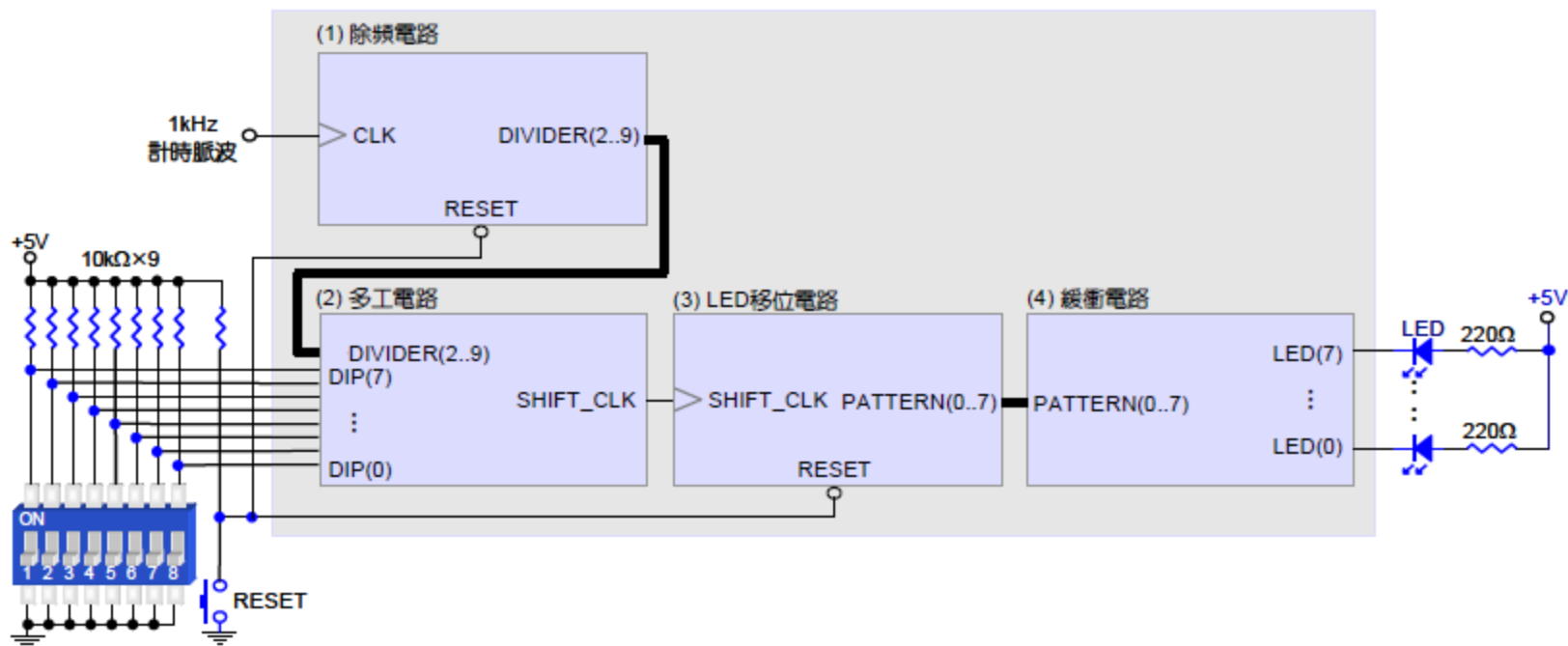


圖9-10 指撥開關控制 LED 移位速度電路方塊圖


```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity DIP8_VAR_SHIFT is
    port
    (
        RESET,CLK:in std_logic;
        DIP:in std_logic_vector(7 downto 0);
        LED:out std_logic_vector(7 downto 0));
end DIP8_VAR_SHIFT;

architecture arch of DIP8_VAR_SHIFT is
    signal DIVIDER:std_logic_vector(9 downto 0);
    signal SHIFT_CLK:std_logic;
    signal PATTERN:std_logic_vector(7 downto 0);
begin

    --divider
    process(CLK,RESET)
    begin
        if RESET='0' then
            DIVIDER<="0000000000";
        elsif CLK'event and CLK='1' then
            DIVIDER<=DIVIDER+1;
        end if;
    end process;

    --multiplxer
    with DIP select
    SHIFT_CLK<=
        DIVIDER(2)  when "0111111",
        DIVIDER(3)  when "1011111",
        DIVIDER(4)  when "1101111",
        DIVIDER(5)  when "1110111",
        DIVIDER(6)  when "1111011",
        DIVIDER(7)  when "1111101",
        DIVIDER(8)  when "1111110",
        DIVIDER(9)  when others;

    --shift circuit
    process(SHIFT_CLK,RESET)
    begin
        if RESET='0' then
            PATTERN<="01111111";
        elsif SHIFT_CLK'event and SHIFT_CLK='1' then
            PATTERN<=PATTERN(0)&PATTERN(7 downto 1);
        end if;
    end process;

    --buffer circuit
    LED<=PATTERN;
end arch;

```

指撥開關控制LED不同變化

□ 功能說明：

使用 CPLD 晶片，設計指撥開關控制 LED 產生單燈右移、單燈左移、閃爍及左右來回移等四種變化的數位電路。當指撥開關 S1 切至 ON 位置時，LED 單燈右移；當指撥開關 S2 切至 ON 位置時，LED 單燈左移；當指撥開關 S3 切至 ON 位置時，LED 閃爍；當指撥開關 S4 切至 ON 位置時，LED 左右來回移。

□ 電路方塊圖：

如圖 9-12 所示為指撥開關控制 LED 變化電路方塊圖，包含除頻電路、LED 右移電路、LED 左移電路、LED 閃爍電路、LED 左右移電路及多工電路等六個部份。

指撥開關控制LED不同變化 (dip8_var_led.vhd)


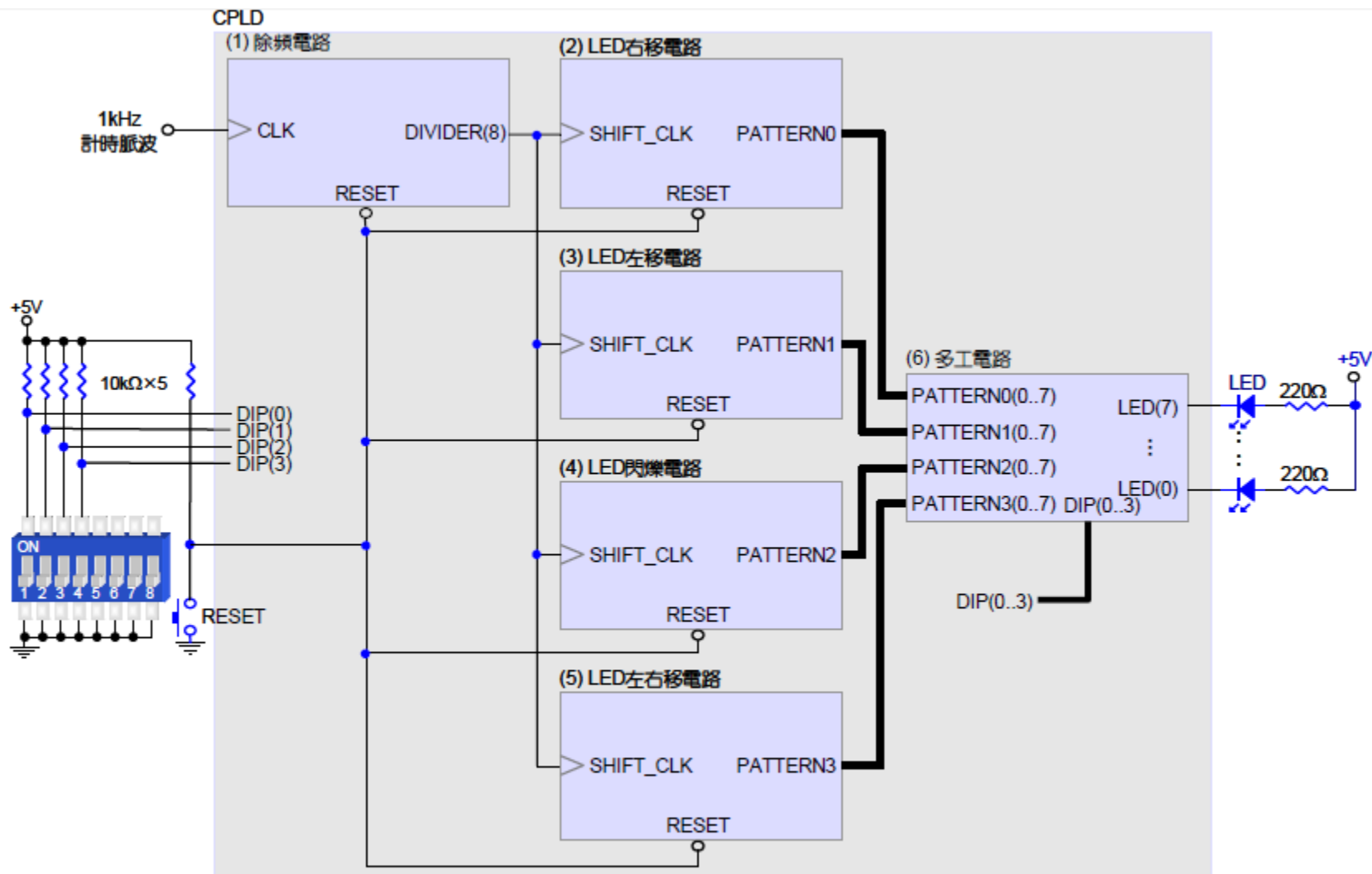


圖9-12 指撥開關控制 LED 變化電路方塊圖


按鍵開關控制LED移位方向

□ 功能說明：

 使用 CPLD 晶片，設計按鍵開關 SW 控制 LED 移位方向的數位電路。按下 RESET 鍵時，執行 LED 單燈右移；每一次按 SW 鍵時，LED 的移位方向會在單燈左移與單燈右移之間改變。



(a) 正脈波型

 

(b) 負脈波型

圖9-14 按鍵開關電路

按鍵開關控制LED移位方向 (tack_sw1_led.vhd)

□ 電路方塊圖：

如圖 9-17 所示為指撥開關控制 LED 移位方向電路方塊圖，包含除頻電路、除彈跳電路、方向控制電路、LED 移位電路等四個部份。

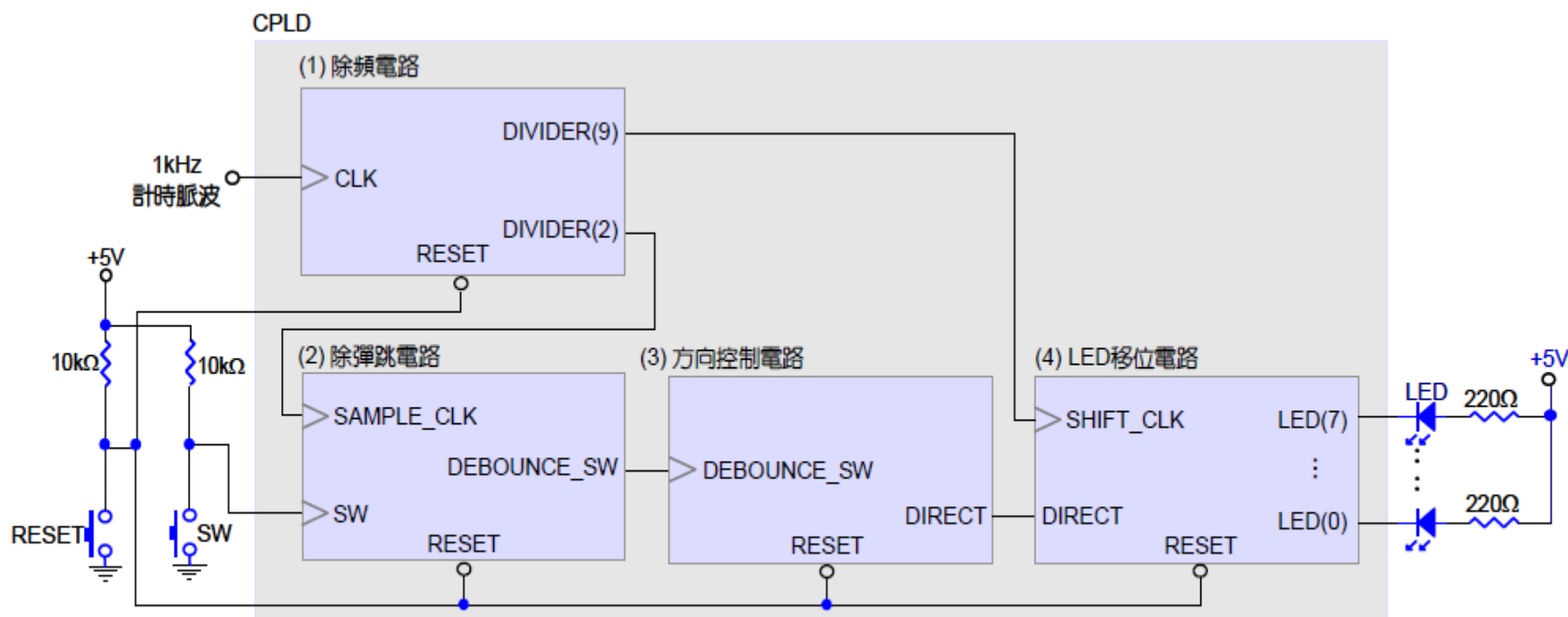


圖9-17 指撥開關控制 LED 移位方向電路方塊圖

按鍵開關控制LED不同變化

□ 功能說明：

使用 CPLD 晶片，設計使用四個按鍵開關控制 LED 產生單燈右移、單燈左移、同時閃爍及左右來回移等四種變化的數位電路。當按下 SW0 鍵時，執行單燈右移動作，按下 SW1 鍵時，執行單燈左移動作，按下 SW2 鍵時，執行閃爍動作，按下 SW3 鍵時，執行左右來回移動作。

□ 電路方塊圖：

如圖 9-19 所示為按鍵開關控制 LED 變化電路方塊圖，包含除頻電路、除彈跳電路、LED 右移電路、LED 左移電路、LED 閃爍電路、LED 左右移電路、多工電路等七個部份。

按鍵開關控制LED不同變化 (tack_sw4_led.vhd)


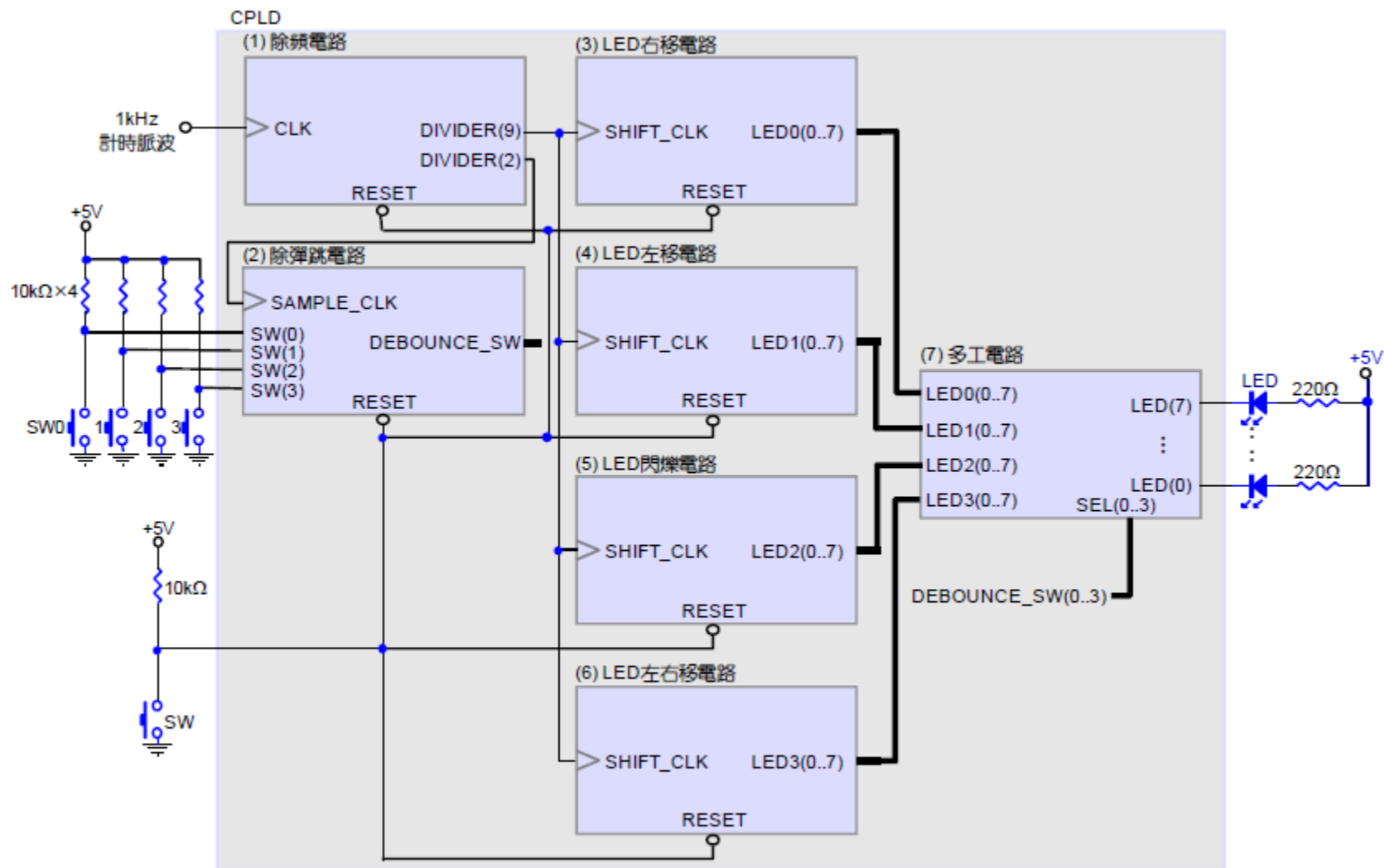


圖9-19 按鍵開關控制 LED 變化電路方塊圖

LEDs Flashing (dip8flash.vhd)

 


⇒ Modified for DE0

```
entity DIP8FLASH is
  port
  (  CLOCK_50:in std_logic;
    KEY:in std_logic_vector(2 downto 0);
    SW:in std_logic_vector(7 downto 0);
    LEDG:out std_logic_vector(7 downto 0));
end DIP8FLASH;
```


Wheel of Fortune




Wheel of Fortune (count_0_9.vhd)

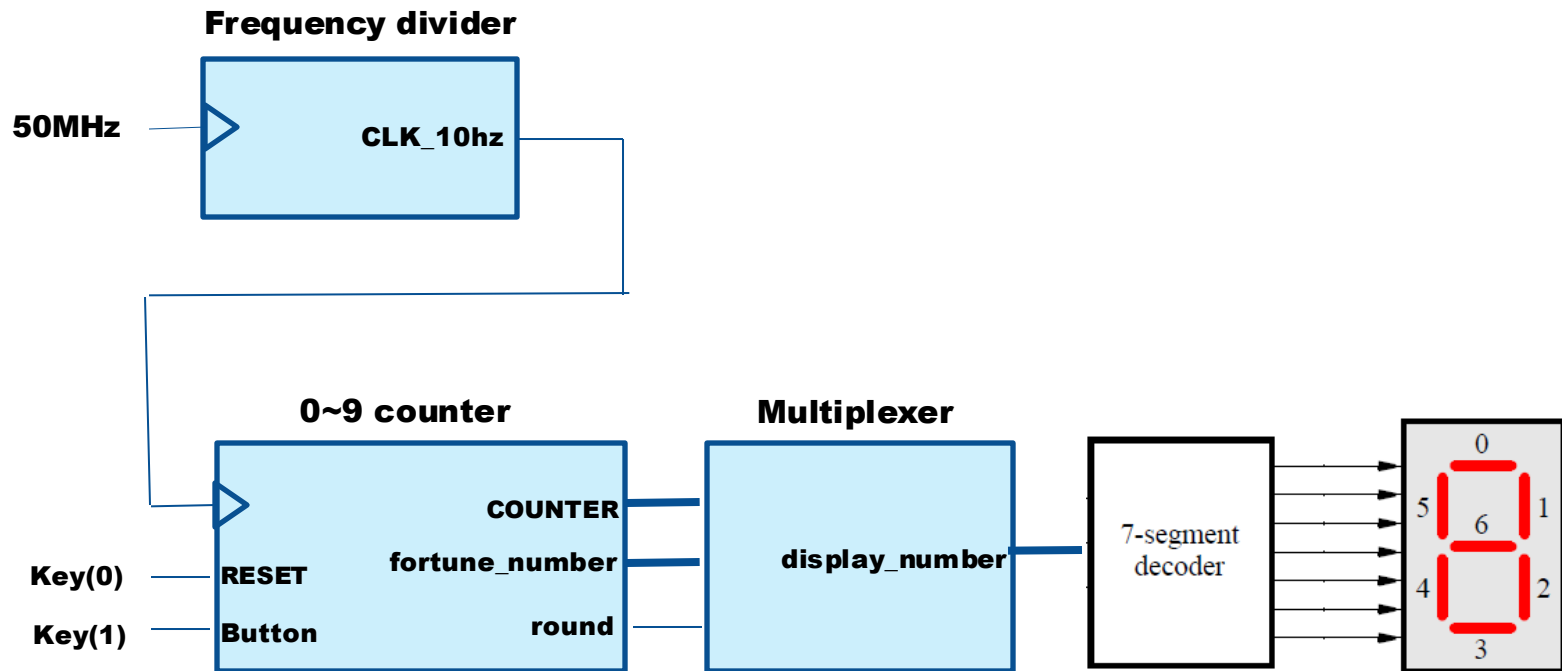


- 按下Key(0), 7-segment 會從數字0開始,快速循環顯示0 ~ 9.
- 在0 ~ 9的數字顯示過程中, 如果按下Key(1), 7-segment 會顯示"幸運數字(固定不變)".
- 再按一次Key(1)的話, 7-segment 會重新快速循環顯示0 ~ 9.

Debounce Circuit

 

Button Debouncing

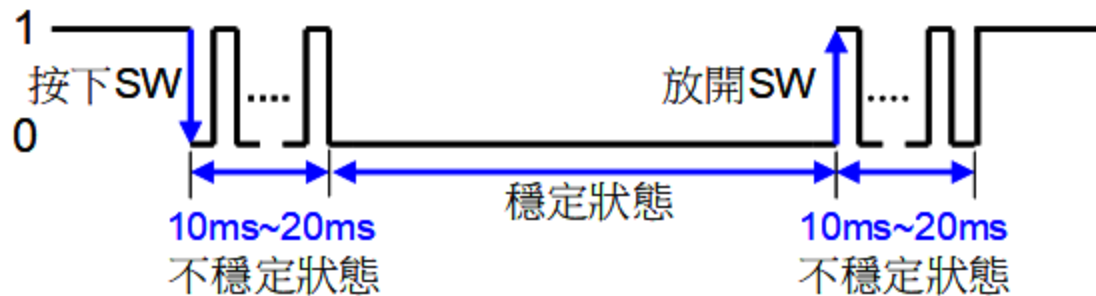


- ◆ **作法一:** 由於一般彈跳時間約在10ms~20ms間，可直接採用較慢的取樣頻率, i.e. $\geq 20\text{ms}$, 取樣(sample)按鍵值.
- ◆ **作法二:** 採用較快的取樣頻率, i.e. $\leq 5\text{ms}$, 先讀取一次，隔一段時間後，再讀取一次。如果持續 n 次 (i.e., $n=5$) 讀到的狀態都一樣，就視為按鍵處於穩定狀態，否則就是 bouncing。
 - An n -bit shift register can be used.
 - Or, the circuit on the following pages will be used.

(Note: DE0 的 pushbuttons 都已 debounce 處理過.)


Debounce Logic Circuit

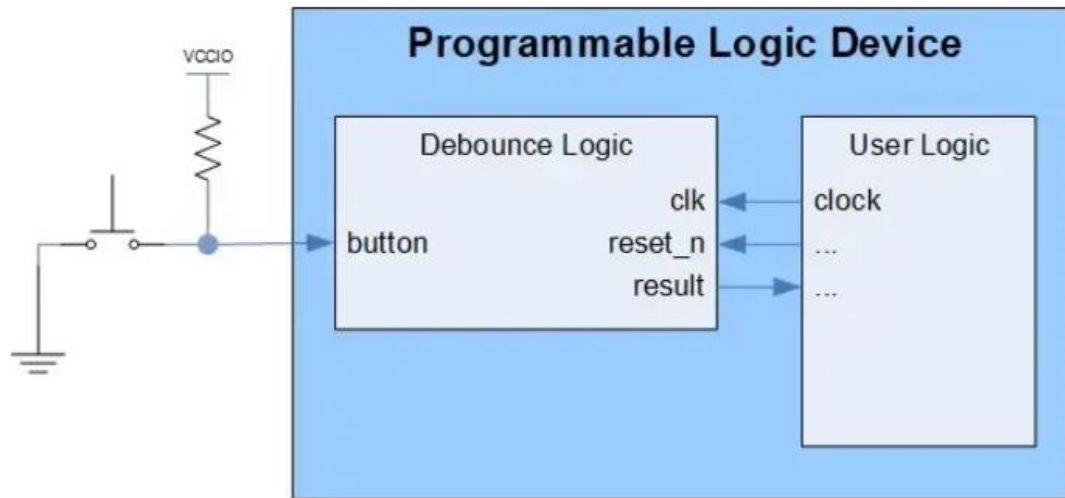- The debounce component presented here is a simple digital logic circuit that addresses this temporary ambiguity (a common task when interfacing FPGAs or CPLDs with pushbuttons or other switches).




Debounce Logic Circuit

- The debounce circuit continuously clocks the button's logic level into FF1 and subsequently into FF2. So, FF1 and FF2 always store **the last two logic levels** of the button.
- When these two values remain identical for a specified time, then FF3 is enabled, and the stable value is clocked through to the result output.
- **If the button's level changes**, the values of FF1 and FF2 differ for a clock cycle, **clearing the counter** via the XOR gate.
- **If the button's level is unchanging** (i.e. if FF1 and FF2 are the same logic level), then the XOR gate releases the counter's synchronous clear, and the counter begins to count.

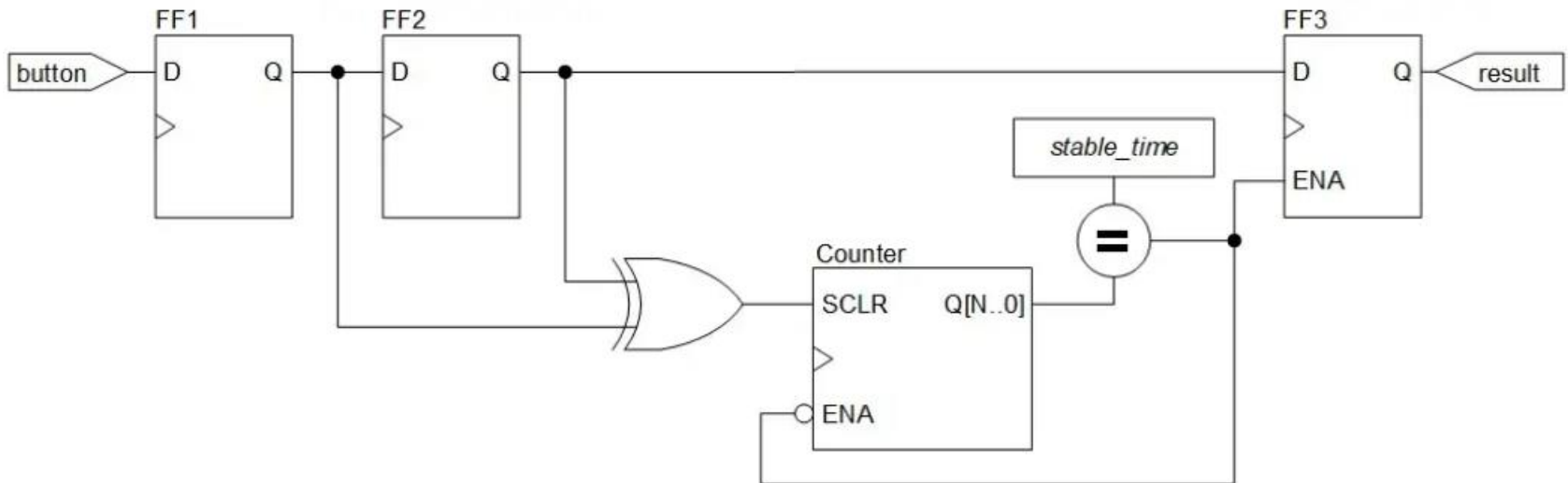

Debounce Logic Circuit

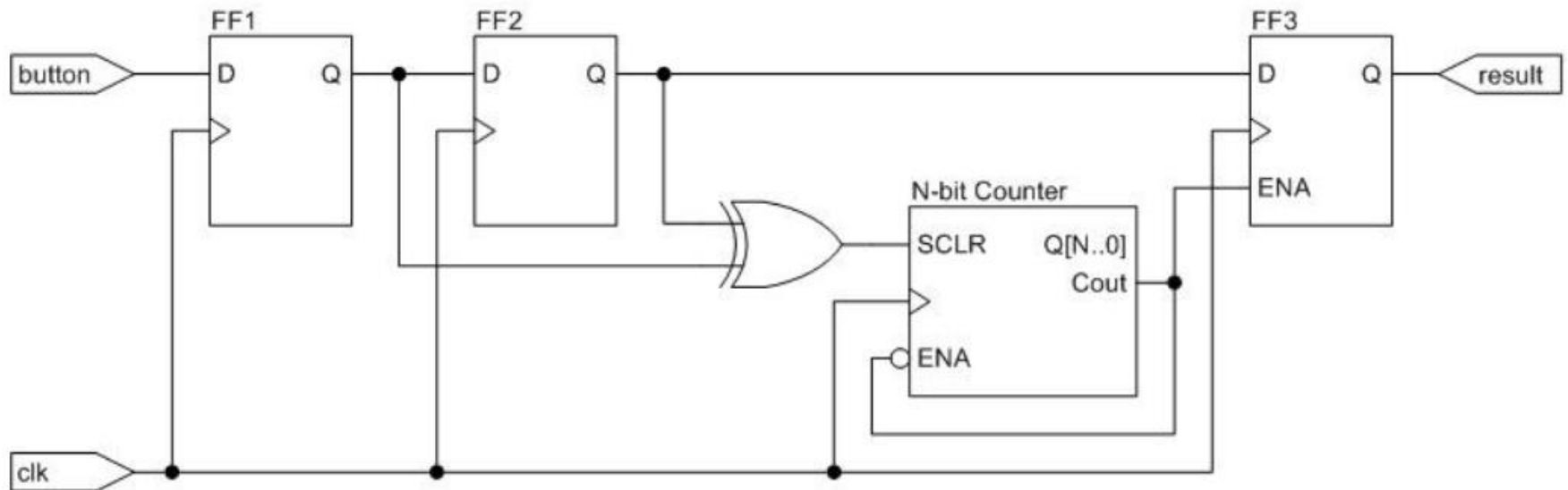- **N-bit Counter** is used to determine the time required to validate the button's stability.
- When **the counter increments to the point that its carry out bit is asserted**, it disables itself from incrementing further and enables the output register FF3.
- The circuit remains in this state until a different button value is clocked into FF1, clearing the counter via the XOR gate.



VHDL for Debounce Logic Circuit

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;

ENTITY debounce IS
    GENERIC(
        counter_size : INTEGER := 19); --counter size (19 bits gives 10.5ms with 50MHz clock)
    PORT(
        clk      : IN  STD_LOGIC; --input clock
        button   : IN  STD_LOGIC; --input signal to be debounced
        result   : OUT STD_LOGIC); --debounced signal
END debounce;

ARCHITECTURE logic OF debounce IS
    SIGNAL flipflops : STD_LOGIC_VECTOR(1 DOWNTO 0); --input flip flops
    SIGNAL counter_set : STD_LOGIC; --sync reset to zero
    SIGNAL counter_out : STD_LOGIC_VECTOR(counter_size DOWNTO 0) := (OTHERS => '0'); --counter output
BEGIN


    counter_set <= flipflops(0) xor flipflops(1); --determine when to start/reset counter

    PROCESS(clk)
    BEGIN
        IF(clk'EVENT and clk = '1') THEN
            flipflops(0) <= button;
            flipflops(1) <= flipflops(0);
            If(counter_set = '1') THEN --reset counter because input is changing
                counter_out <= (OTHERS => '0');
            ELSIF(counter_out(counter_size) = '0') THEN --stable input time is not yet met
                counter_out <= counter_out + 1;
            ELSE --stable input time is met
                result <= flipflops(1);
            END IF;
        END IF;
    END PROCESS;
END logic;
```



8x8 LED Matrix Control



8x8 LED Matrix

  


(a) 共陰型(CC)




(b) 共陽型(CA)

8x8 LED Matrix – static display

 


(以行掃描為例做說明)


<多工掃描>

 


(a) 第 1 次掃描

 


(b) 第 2 次掃描

 


(c) 第 3 次掃描

 


(d) 第 4 次掃描

 


(e) 第 5 次掃描

 

(f) 第 6 次掃描

 


(g) 第 7 次掃描

 

(h) 第 8 次掃描



8x8 LED Matrix

◆ 實驗所用為 1088AS

 


front-side

back-side

  


8x8 LED Matrix – static display

⇒ led8x8static.vhd

 


(以列掃描為例做說明)


<多工掃描>

 


(a) 第 1 次掃描

 


(b) 第 2 次掃描

 


(c) 第 3 次掃描

 


(d) 第 4 次掃描

 


(e) 第 5 次掃描

 

(f) 第 6 次掃描

 


(g) 第 7 次掃描


 


(h) 第 8 次掃描

8x8 LED Matrix – connect to DE0 GPIOs

 


8x8 LED Matrix – connect to DE0 GPIOs

 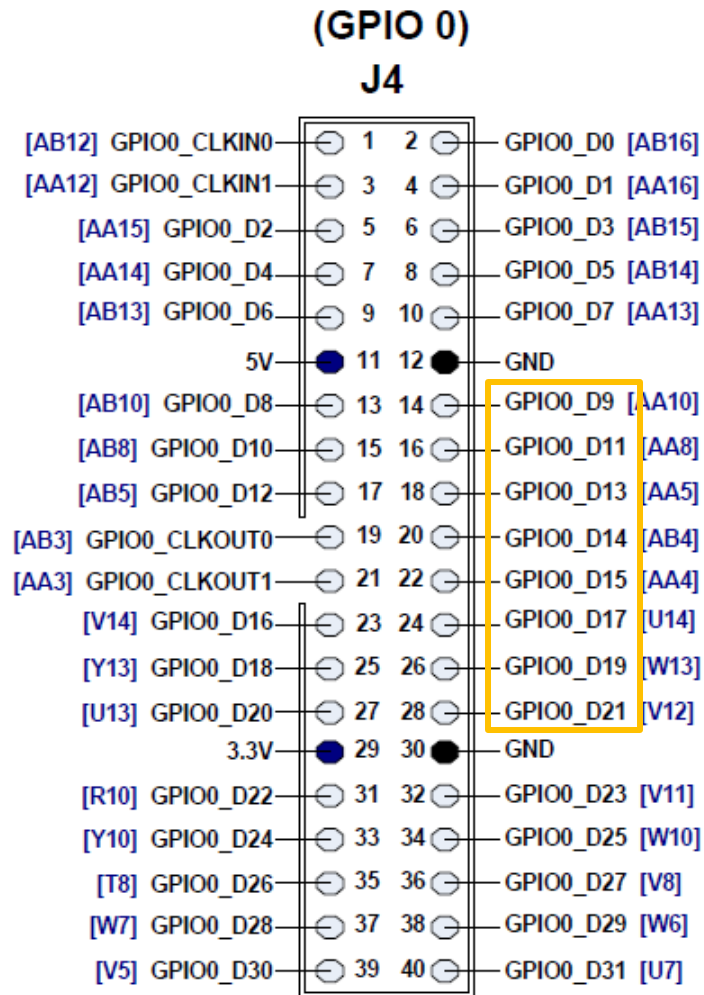

8x8 LED Matrix- dynamic display

⇒ led8x8shift.vhd

左移

 

右移

