
Digital System Design

Lecture 7

Finite State Machines

- **Reading Assignment:**

- Brown, “Fundamentals of Digital Logic with VHDL,
pp. 485 - 519

- **Learning Objective:**

- Modeling sequential logic using the behavioral modeling techniques.
- Design VHDL behavioral models for Moore and Mealy finite-state machines

Learning Examples:

- **A Simple Sequence Recognizer (Moore)**
- **A Simple Sequence Recognizer (Mealy)**
- **A Gray-code counter**
- **An Arbiter**
- **A Serial Adder (Mealy)**
- **A Serial Adder (Moore)**

Overview

- “State machine” (or “finite state machine”) is a generic name given to sequential circuits
- “Clocked” indicates that the flip-flops employ a CLOCK (CLK) input
- “Synchronous” means that all the flip-flops in the state machine use the same CLOCK signal
- “Analysis” means to analyze the behavior of a given state machine
 - construct a PS-NS table
 - derive PS-NS equations
 - draw a state transition diagram
 - draw a timing chart

State Machine Structure


Clocked synchronous state machines consist of three basic blocks:

- **next state logic** – combinational circuitry that provides the “excitation” necessary to transition to the next state, based on the current state and the present inputs
- **state memory (flip flops)** – set of N flip-flops that store the current state of the machine (providing 2^N distinct states)
- **output logic** – combinational circuitry that uses the current state (and possibly current inputs) to determine the outputs generated

Machine Structures


In a **Moore** machine, the **outputs** are only a function of the **current state**

Moore Machine

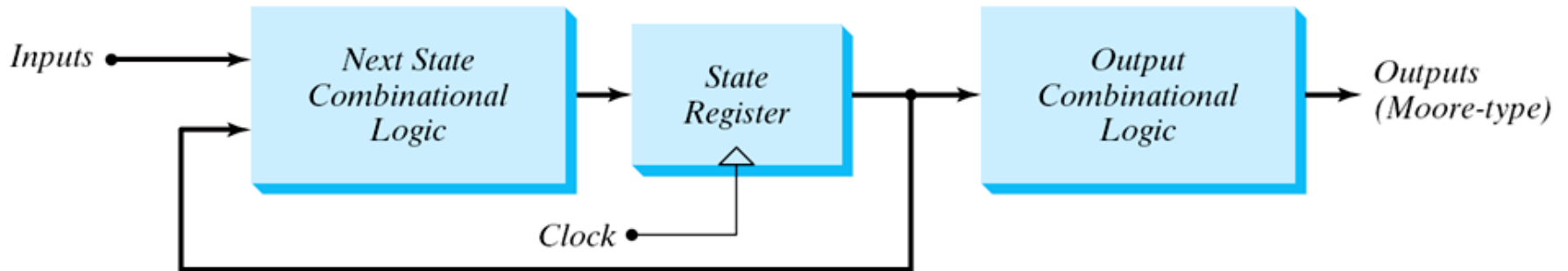


In a **Mealy** machine, the **outputs** are a function of the **current state** as well as the **current inputs**

Mealy Machine

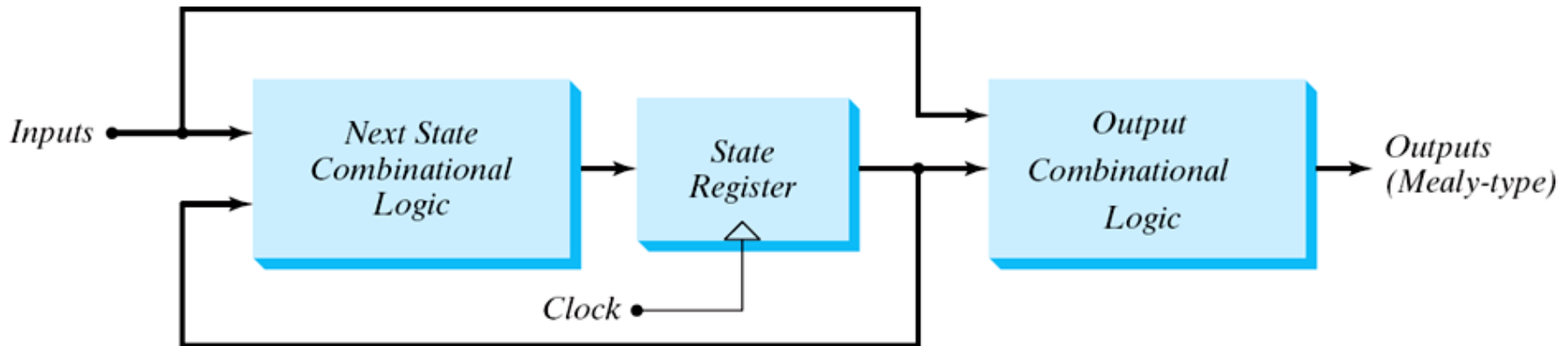

 Example – A Simple Sequence Recognizer (Moore)

- Circuit has one input, w , and one output, z .
- Changes occur on positive clock edge.
- z is 1 if w is 1 during last two clock cycles.




Example – A Simple Sequence Recognizer (Moore)

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

	Present state	Next state		Output z
		$w = 0$	$w = 1$	
	$y_2 y_1$	$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

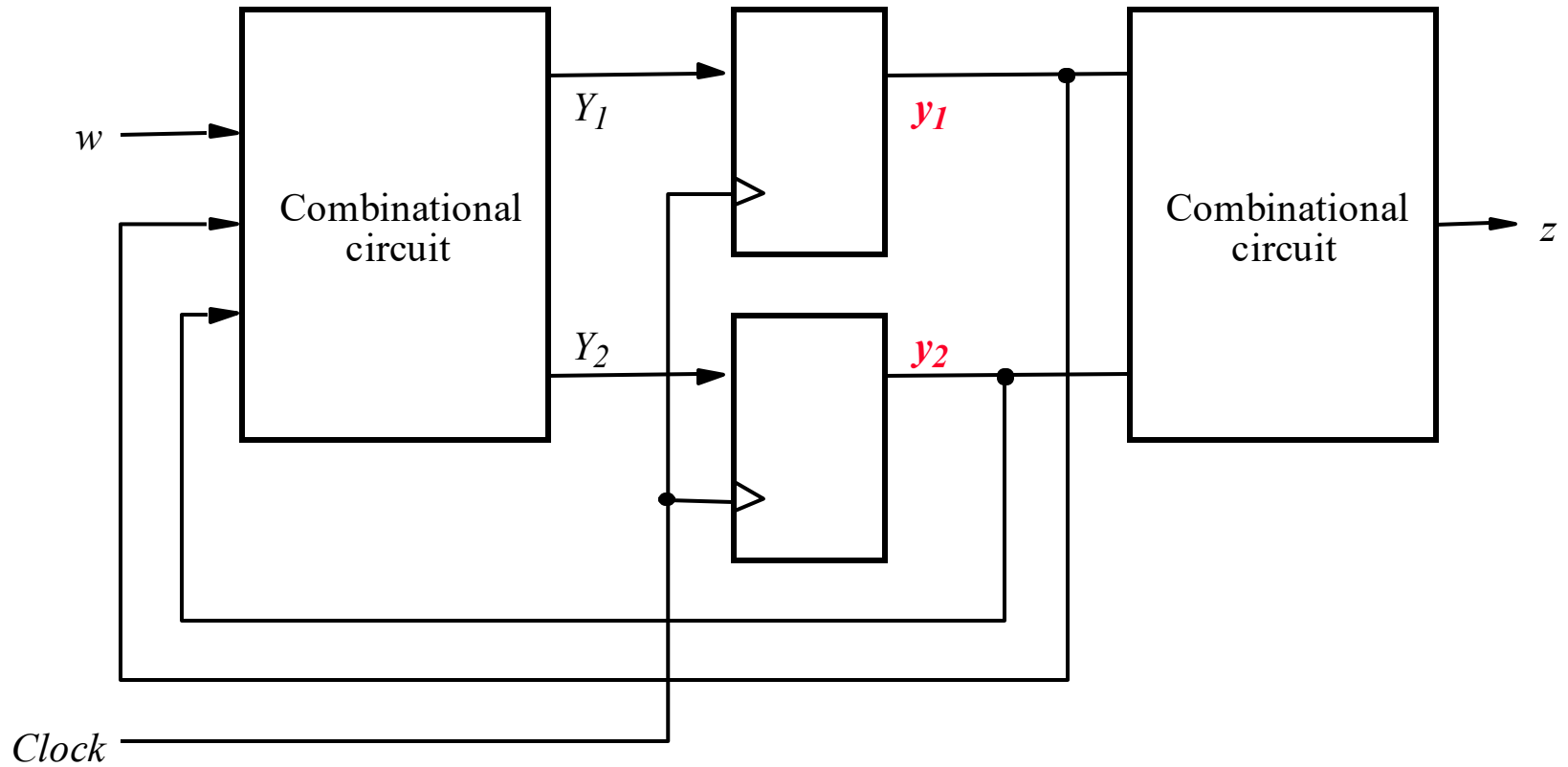Example – A Simple Sequence Recognizer (Moore)



Example – A Simple Sequence Recognizer (Moore)

$y_2 y_1$		00	01	11	10
w	0	0	0	d	0
	1	1	0	d	0

Ignoring don't cares

$$Y_1 = w\bar{y}_1\bar{y}_2$$

Using don't cares

$$Y_1 = w\bar{y}_1\bar{y}_2$$

$y_2 y_1$		00	01	11	10
w	0	0	0	d	0
	1	0	1	d	1

$$Y_2 = wy_1\bar{y}_2 + w\bar{y}_1y_2$$


$$\begin{aligned} Y_2 &= wy_1 + wy_2 \\ &= w(y_1 + y_2) \end{aligned}$$

y_2	y_1	
	0	1
0	0	0
1	1	d


$$z = \bar{y}_1y_2$$

$$z = y_2$$

 Example –A Simple Sequence Recognizer (Moore)



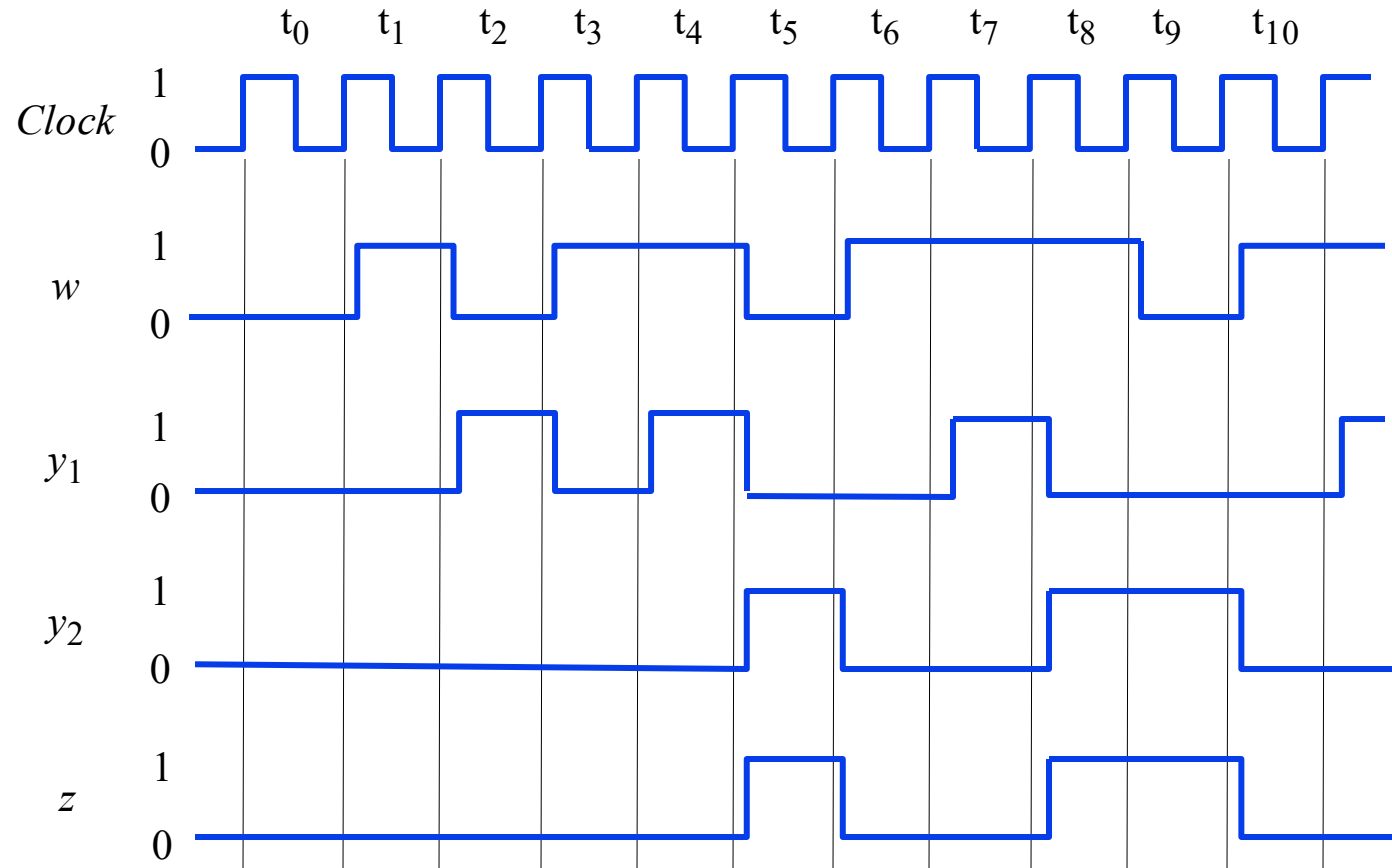
Example – A Simple Sequence Recognizer (Moore)



Example – A Simple Sequence Recognizer (Moore)

● Improved state assignment

	Present state $y_2 y_1$	Next state		Output z
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	dd	dd	d

 

● One-hot state assignment

	Present state $y_3 y_2 y_1$	Nextstate		Output z
		$w = 0$	$w = 1$	
		$Y_3 Y_2 Y_1$	$Y_3 Y_2 Y_1$	
A	001	001	010	0
B	010	001	100	0
C	100	001	100	1

VHDL code for a Simple Sequence Recognizer (Moore)

```
USE ieee.std_logic_1164.all;
```

```
ENTITY simple IS
```

```
    PORT ( Clock, Resetn, w : IN      STD_LOGIC ;  
           z                  : OUT    STD_LOGIC ) ;
```

```
END simple ;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    TYPE State_type IS (A, B, C) ;
```

```
    SIGNAL y : State_type ;
```

```
BEGIN
```

```
    PROCESS ( Resetn, Clock )
```

```
    BEGIN
```

```
        IF Resetn = '0' THEN
```

```
            y <= A ;
```

```
        ELSIF (Clock'EVENT AND Clock = '1') THEN
```

```
            CASE y IS
```

```
                WHEN A =>
```

```
                    IF w = '0' THEN
```

```
                        y <= A ;
```

```
                    ELSE
```

```
                        y <= B ;
```

```
                    END IF ;
```

```
                WHEN B =>
```

```
                    IF w = '0' THEN
```

```
                        y <= A ;
```

```
                    ELSE
```

```
                        y <= C ;
```

```
                    END IF ;
```

```
                WHEN C =>
```

```
                    IF w = '0' THEN
```

```
                        y <= A ;
```

```
                    ELSE
```

```
                        y <= C ;
```

```
                    END IF ;
```

```
            END CASE ;
```

```
        END IF ;
```

```
    END PROCESS ;
```

```
    z <= '1' WHEN y = C ELSE '0' ;
```

```
END Behavior ;
```

A Better VHDL code for a Simple Sequence Recognizer

(ENTITY declaration not shown)

ARCHITECTURE Behavior OF simple IS

TYPE State_type IS (A, B, C) ;

SIGNAL y_present, y_next : State_type ;

BEGIN

PROCESS (w, y_present) -- next state logic

BEGIN

CASE y_present IS

WHEN A =>

IF w = '0' THEN

y_next <= A ;

ELSE

y_next <= B ;

END IF ;

WHEN B =>

IF w = '0' THEN

y_next <= A ;

ELSE

y_next <= C ;

END IF ;

A Better VHDL code for a Simple Sequence Recognizer

```
        WHEN C =>
            IF w = '0' THEN
                y_next <= A ;
            ELSE
                y_next <= C ;
            END IF ;
        END CASE ;
    END PROCESS ;

    PROCESS (Clock, Resetn)          -- state memory
    BEGIN
        IF Resetn = '0' THEN
            y_present <= A ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            y_present <= y_next ;
        END IF ;
    END PROCESS ;

    z <= '1' WHEN y_present = C ELSE '0' ;    -- output logic
END Behavior ;
```


A user-defined attribute for manual state assignment

(ENTITY declaration not shown)

ARCHITECTURE Behavior OF simple IS

TYPE State_TYPE IS (A, B, C) ;

ATTRIBUTE ENUM_ENCODING : STRING ;

ATTRIBUTE ENUM_ENCODING OF State_type : TYPE IS "00 01 11" ;

SIGNAL y_present, y_next : State_type ;

BEGIN

con't ...

Using constants for manual state assignment

```
LIBRARY ieee ;
```

```
USE ieee.std_logic_1164.all ;
```

```
ENTITY simple IS
```

```
    PORT (    Clock, Resetn, w      : IN  STD_LOGIC ;  
            z                        : OUT  STD_LOGIC ) ;
```

```
END simple ;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    SIGNAL y_present, y_next : STD_LOGIC_VECTOR(1 DOWNTO 0);
```

```
    CONSTANT A : STD_LOGIC_VECTOR(1 DOWNTO 0) := "00" ;
```

```
    CONSTANT B : STD_LOGIC_VECTOR(1 DOWNTO 0) := "01" ;
```

```
    CONSTANT C : STD_LOGIC_VECTOR(1 DOWNTO 0) := "11" ;
```

```
BEGIN
```

```
    PROCESS ( w, y_present )    -- next state logic
```

```
    BEGIN
```

```
        CASE y_present IS
```

```
            WHEN A =>
```

```
                IF w = '0' THEN y_next <= A ;
```

```
                ELSE y_next <= B ;
```

```
                END IF ;
```

... con't

Using constants for manual state assignment


```
    WHEN B =>
        IF w = '0' THEN y_next <= A ;
        ELSE y_next <= C ;
        END IF ;
    WHEN C =>
        IF w = '0' THEN y_next <= A ;
        ELSE y_next <= C ;
        END IF ;
    WHEN OTHERS =>
        y_next <= A ;
    END CASE ;
END PROCESS ;

PROCESS ( Clock, Resetn )    -- state memory
BEGIN
    IF Resetn = '0' THEN
        y_present <= A ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next ;
    END IF ;
END PROCESS ;

z <= '1' WHEN y_present = C ELSE '0' ;    -- output logic

END Behavior ;
```

 Example – A Simple Sequence Recognizer (Mealy)




Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Example – A Simple Sequence Recognizer (Mealy)


Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

 Example – A Simple Sequence Recognizer (Mealy)



(a) Circuit

 

(b) Timing diagram

VHDL code for a Simple Sequence Recognizer (Mealy)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mealy IS
    PORT ( Clock, Resetn, w      : IN    STD_LOGIC ;
          z                      : OUT   STD_LOGIC ) ;
END mealy ;

ARCHITECTURE Behavior OF mealy IS
    TYPE State_type IS (A, B) ;
    SIGNAL y_present, y_next : State_type ;
BEGIN
    PROCESS ( w, y_present )    -- next state logic
    BEGIN
        CASE y_present IS
            WHEN A =>
                IF w = '0' THEN y_next <= A ;
                ELSE y_next <= B ;
                END IF ;
            WHEN B =>
                IF w = '0' THEN y_next <= A ;
                ELSE y_next <= B ;
                END IF ;
        END CASE ;
    END PROCESS ;
```

VHDL code for a Simple Sequence Recognizer (Mealy)

```
PROCESS ( Clock, Resetn )    -- state memory
BEGIN
    IF Resetn = '0' THEN
        y_present <= A ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next ;
    END IF ;
END PROCESS ;

PROCESS (w, y_present )      -- output logic
BEGIN
    CASE y_present IS
        WHEN A =>
            z <= '0' ;
        WHEN B =>
            z <= w ;
    END CASE ;
END PROCESS ;
END Behavior ;
```


Example – Gray-code counter

Design an FSM that realizes a three-bit Gray-code counter, which counts in the sequence

000, 001, 011, 010, 110, 111, 101, 100, 000,

- If $w = 0$, the present count remains the same; if $w = 1$, the count is incremented

State table (Moore Machine)

Present state	Next state		Output $z_2 z_1 z_0$
	$w = 0$	$w = 1$	
A	A	B	0 0 0
B	B	C	0 0 1
C	C	D	0 1 1
D	D	E	0 1 0
E	E	F	1 1 0
F	F	G	1 1 1
G	G	H	1 0 1
H	H	A	1 0 0

VHDL for Gray-code counter

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY prob8_45 IS
    PORT ( Clock, Resetn, w : IN STD_LOGIC ;
          z : OUT STD_LOGIC_VECTOR(2 DOWNTO 0) ) ;
END prob8_45 ;

ARCHITECTURE Behavior OF prob8_45 IS
    SIGNAL y_present, y_next : STD_LOGIC_VECTOR(2 DOWNTO 0);
    CONSTANT A : STD_LOGIC_VECTOR(2 DOWNTO 0) := "000" ;
    CONSTANT B : STD_LOGIC_VECTOR(2 DOWNTO 0) := "001" ;
    CONSTANT C : STD_LOGIC_VECTOR(2 DOWNTO 0) := "011" ;
    CONSTANT D : STD_LOGIC_VECTOR(2 DOWNTO 0) := "010" ;
    CONSTANT E : STD_LOGIC_VECTOR(2 DOWNTO 0) := "110" ;
    CONSTANT F : STD_LOGIC_VECTOR(2 DOWNTO 0) := "111" ;
    CONSTANT G : STD_LOGIC_VECTOR(2 DOWNTO 0) := "101" ;
    CONSTANT H : STD_LOGIC_VECTOR(2 DOWNTO 0) := "100" ;

    ... con't
```

VHDL for Gray-code counter

```
BEGIN
  PROCESS ( w, y_present )
  BEGIN
    CASE y_present IS
      WHEN A =>
        IF w = '0' THEN y_next <= A ;
        ELSE y_next <= B ;
        END IF ;
      WHEN B =>
        IF w = '0' THEN y_next <= B ;
        ELSE y_next <= C ;
        END IF ;
      WHEN C =>
        IF w = '0' THEN y_next <= C ;
        ELSE y_next <= D ;
        END IF ;
      WHEN D =>
        IF w = '0' THEN y_next <= D ;
        ELSE y_next <= E ;
        END IF ;
      WHEN E =>
        IF w = '0' THEN y_next <= E ;
        ELSE y_next <= F ;
        END IF ;
      WHEN F =>
        IF w = '0' THEN y_next <= F ;
        ELSE y_next <= G ;
        END IF ;
      WHEN G =>
        IF w = '0' THEN y_next <= G ;
        ELSE y_next <= H ;
        END IF ;
      WHEN H =>
        IF w = '0' THEN y_next <= H ;
        ELSE y_next <= A ;
        END IF ;
    END CASE ;
  END PROCESS ;

  PROCESS ( Clock, Resetn )
  BEGIN
    IF Resetn = '0' THEN
      y_present <= A ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
      y_present <= y_next ;
    END IF ;
  END PROCESS ;


  z <= y_present ;
END Behavior ;
```

Example – An Arbiter Circuit


The purpose of the machine is to control access by various devices to a shared resource in a given system.

- Only one device can use the resource at a time.
 - Each device provides one input to the FSM, called a *request*. A device indicates its need to use the resource by asserting its request signal.
 - FSM produces a separate output for each device, called a *grant*.
 - Based on a priority scheme, it selects one of the requesting devices and asserts its grant signal. When the device is finished using the resource, it de-asserts its request signal.
-
- We will assume that there are three devices in the system, called device 1, device 2, and device 3.
 - The request signals are named r_1 , r_2 , and r_3 , and the grant signals are called g_1 , g_2 , and g_3 .
 - Priority: device 1 > device 2 > device 3

State Diagram for the Arbiter

 

 Alternative style of State Diagram for the Arbiter



VHDL for the Arbiter

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY arbiter IS
    PORT (   Clock, Resetn   : IN    STD_LOGIC ;
            r                 : IN    STD_LOGIC VECTOR(1 TO 3) ;
            g                 : OUT   STD_LOGIC VECTOR(1 TO 3) ) ;
END arbiter ;

ARCHITECTURE Behavior OF arbiter IS
    TYPE State_type IS (Idle, gnt1, gnt2, gnt3) ;
    SIGNAL y_present, y_next : State_type ;
BEGIN
    PROCESS ( r, y_present )      -- next state logic
    BEGIN
        CASE y_present IS
            WHEN Idle =>
                IF r(1) = '1'      THEN      y_next <= gnt1 ;
                ELSIF r(2) = '1'  THEN      y_next <= gnt2 ;
                ELSIF r(3) = '1'  THEN      y_next <= gnt3 ;
                ELSE                y_next <= Idle ;
                END IF ;
            WHEN gnt1 =>
                IF r(1) = '1'      THEN      y_next <= gnt1 ;
                ELSE                y_next <= Idle ;
                END IF ;
        END CASE
    END PROCESS
END Behavior
```

VHDL for the Arbiter

```
        WHEN gnt2 =>
            IF r(2) = '1'      THEN      y_next <= gnt2 ;
            ELSE                y_next <= Idle ;
            END IF ;
        WHEN gnt3 =>
            IF r(3) = '1'      THEN      y_next <= gnt3 ;
            ELSE                y_next <= Idle ;
            END IF ;
    END CASE ;
END PROCESS ;


PROCESS (Clock, Resetn)      -- state memory
BEGIN
    IF Resetn = '0' THEN
        y_present <= Idle ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next ;
    END IF ;
END PROCESS ;

g(1) <= '1' WHEN y_present = gnt1 ELSE '0' ;      -- output logic
g(2) <= '1' WHEN y_present = gnt2 ELSE '0' ;
g(3) <= '1' WHEN y_present = gnt3 ELSE '0' ;

END Behavior ;
```

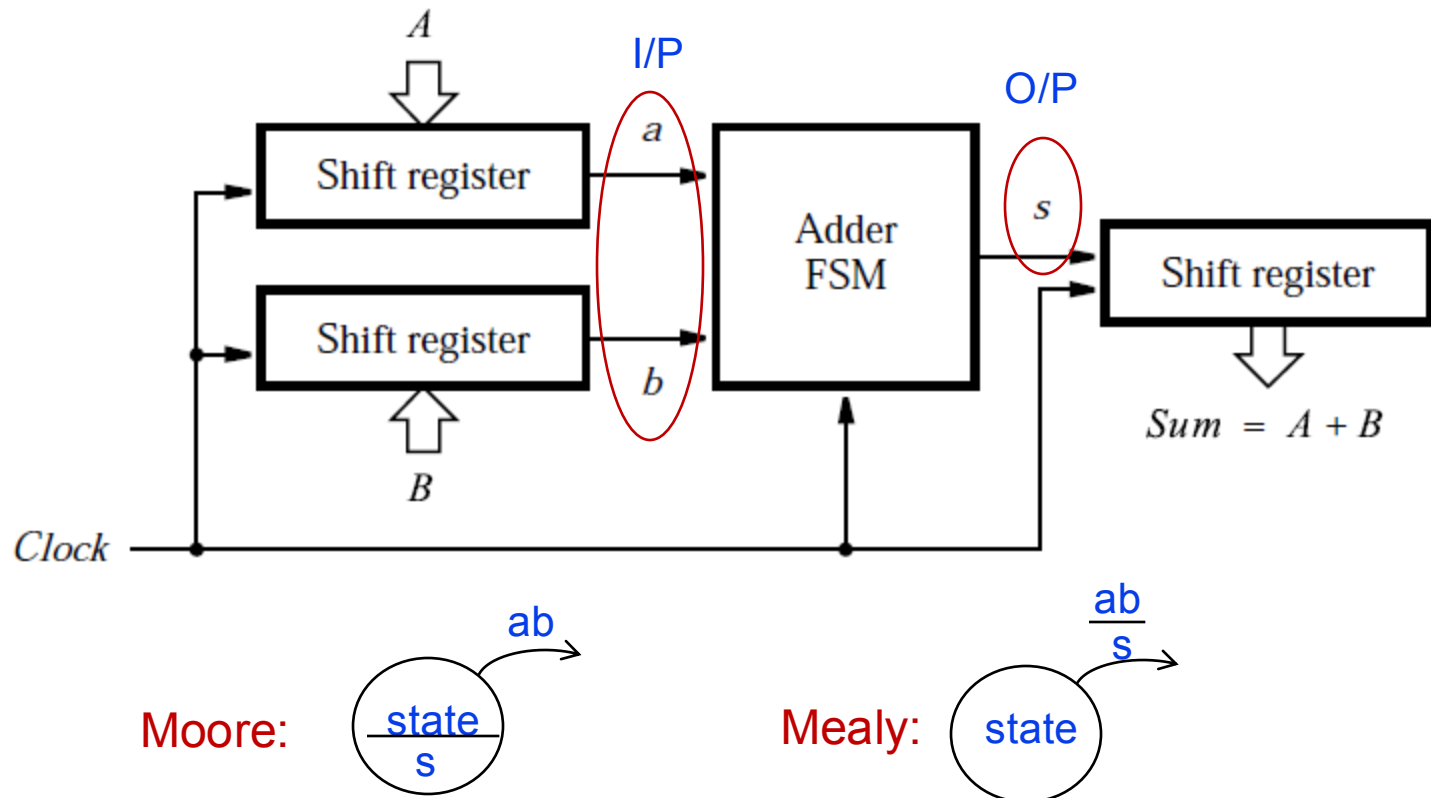 

Example – Serial Adder

- $A = a_{n-1}a_{n-2} \cdots a_0$ and $B = b_{n-1}b_{n-2} \cdots b_0$ be two unsigned numbers that have to be added to produce $\text{Sum} = s_{n-1}s_{n-2} \cdots s_0$
- The addition task begins by loading the values of A and B into shift registers. Then in each clock cycle, a pair of bits is added by the adder FSM, and at the end of the cycle the resulting sum bit is shifted into the Sum register.



Serial Adder (Mealy FSM)

- Two states are needed: let **G** and **H** denote the states where the carry-in values are **0** and **1**, respectively
- Each transition is labeled using the notation **ab/s**, which indicates the value of **s** for a given valuation **ab**



Present state	Next state				Output <i>s</i>			
	<i>ab</i> = 00	01	10	11	00	01	10	11
G	G	G	G	H	0	1	1	0
H	G	H	H	H	1	0	0	1

VHDL for Serial Adder (Mealy FSM)

Code for a left-to-right shift register with an enable input

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

-- left-to-right shift register with parallel load and enable
ENTITY shiftrne IS
    GENERIC ( N : INTEGER := 4 ) ;
    PORT ( R      : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
          L, E, w : IN      STD_LOGIC ;
          Clock   : IN      STD_LOGIC ;
          Q       : BUFFER STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END shiftrne ;

ARCHITECTURE Behavior OF shiftrne IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF E = '1' THEN
            IF L = '1' THEN
                Q <= R ;
            ELSE
                Genbits: FOR i IN 0 TO N-2 LOOP
                    Q(i) <= Q(i+1);
                END LOOP ;
                Q(N-1) <= w ;
            END IF ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

VHDL for Serial Adder (Mealy FSM)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY serial IS
    GENERIC ( length : INTEGER := 8 ) ;
    PORT ( Clock : IN          STD_LOGIC ;
          Reset  : IN          STD_LOGIC ;
          A, B   : IN          STD_LOGIC_VECTOR(length-1 DOWNT0 0) ;
          Sum    : BUFFER STD_LOGIC_VECTOR(length-1 DOWNT0 0) );
END serial ;

ARCHITECTURE Behavior OF serial IS
    COMPONENT shiftrne
        GENERIC ( N : INTEGER := 4 ) ;
        PORT( R      : IN          STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
              L, E, w : IN          STD_LOGIC ;
              Clock   : IN          STD_LOGIC ;
              Q       : BUFFER STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
    END COMPONENT ;

    SIGNAL QA, QB, Null_in : STD_LOGIC_VECTOR(length-1 DOWNT0 0) ;
    SIGNAL s, Low, High, Run : STD_LOGIC ;
    SIGNAL Count : INTEGER RANGE 0 TO length ;
    TYPE State_type IS (G, H) ;
    SIGNAL y : State_type ;
```

VHDL for Serial Adder (Mealy FSM)

```
BEGIN
    Low <= '0' ; High <= '1' ;
    ShiftA: shiftrne GENERIC MAP (N => length)
        PORT MAP ( A, Reset, High, Low, Clock, QA ) ;
    ShiftB: shiftrne GENERIC MAP (N => length)
        PORT MAP ( B, Reset, High, Low, Clock, QB ) ;

    AdderFSM: PROCESS ( Reset, Clock )
    BEGIN
        IF Reset = '1' THEN
            y <= G ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            CASE y IS
                WHEN G =>
                    IF QA(0) = '1' AND QB(0) = '1' THEN y <= H ;
                    ELSE y <= G ;
                    END IF ;
                WHEN H =>
                    IF QA(0) = '0' AND QB(0) = '0' THEN y <= G ;
                    ELSE y <= H ;
                    END IF ;
            END CASE ;
        END IF ;
    END PROCESS AdderFSM ;
```

VHDL for Serial Adder (Mealy FSM)

```
WITH y SELECT
```

```
  s <= QA(0) XOR QB(0)      WHEN G,  
      NOT ( QA(0) XOR QB(0) ) WHEN H ;
```

```
Null_in <= (OTHERS => '0') ;
```

```
ShiftSum: shiftrne GENERIC MAP ( N => length )
```

```
  PORT MAP ( Null_in, Reset, Run, s, Clock, Sum ) ;
```



```
Stop: PROCESS
```

```
BEGIN
```

```
  WAIT UNTIL (Clock'EVENT AND Clock = '1') ;
```

```
  IF Reset = '1' THEN
```

```
    Count <= length ;
```

```
  ELSIF Run = '1' THEN
```

```
    Count <= Count - 1 ;
```

```
  END IF ;
```

```
END PROCESS ;
```

```
Run <= '0' WHEN Count = 0 ELSE '1' ;    -- stops counter and ShiftSum
```

```
END Behavior ;
```

Serial Adder (Moore FSM)

- We will use G_0 and G_1 to denote the fact that the **carry is 0** and that the sum is either 0 or 1, respectively.
- Similarly, we will use H_0 and H_1 to denote the fact that the **carry is 1** and that the sum is either 0 or 1, respectively.

