

## Lab 5- Combinational Circuits ( III ): Using “Component”

The goal of this lab is to design combinational circuits using component and port-map statements. This design style is useful in hierarchical design for large circuits.


### Lab 5.1:

#### A 4-bit key-controlled arithmetic circuit.

Given two 4-bit **signed** binary numbers A and B, a key-controlled arithmetic circuit is operated as follows,

- When Button0 is pushed, decimal value of  $A+B$  is shown on 7-segment displays.
  - When Button1 is pushed, decimal value of  $A-B$  is shown on 7-segment displays.
  - When Button2 is pushed, decimal value of  $A*B$  is shown on 7-segment displays.
  - If the arithmetic result is **negative**, LEDG[9] is ON.
  - For other cases, nothing is displayed.
- To avoid overflow, be sure to declare enough bits for the arithmetic operations in your code. For example, read in A and extend its sign-bit.
  - This time, you are **required** to build a (BCD) 7-segment decoder first, and use it as a component in your design. (Practice the usage of **component** and **port map**.)

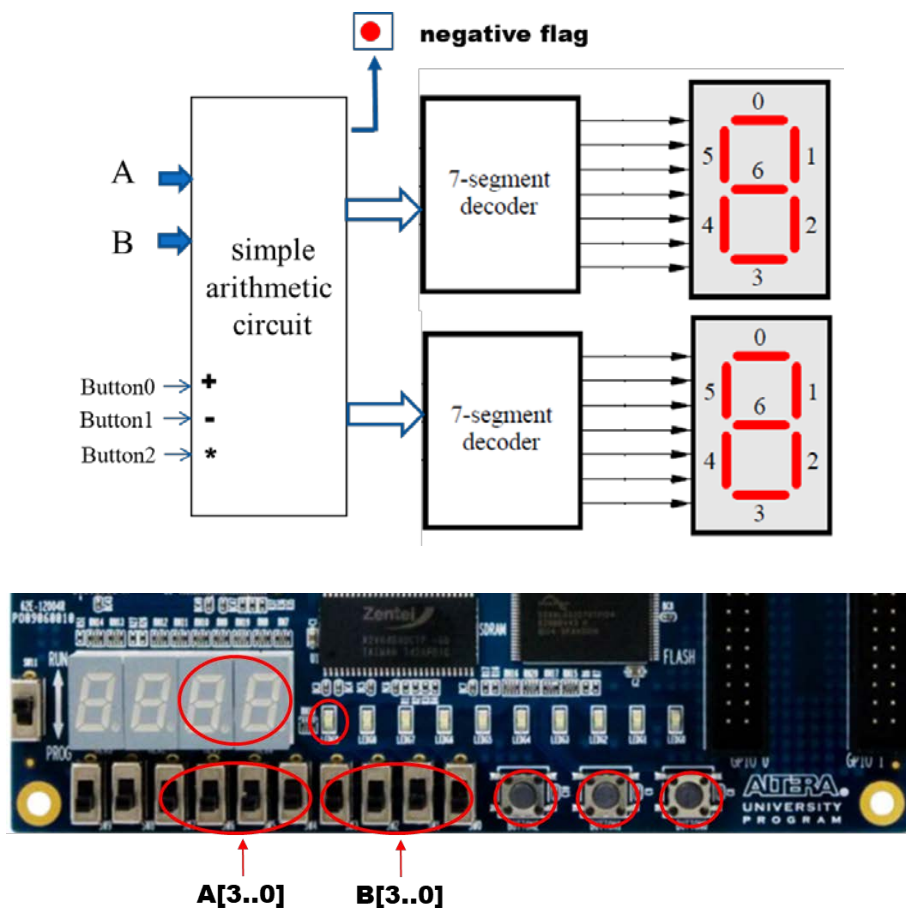**Tip:** One way to do binary arithmetic is to convert signed number to integer first, do computation, and then convert back to signed number.



### Lab-report:

Submit a lab report on **ilearn** by 11:00pm the day before of next lab. (The lab report must be a **PDF** file.) Your Lab report should include the following items:

- 1) VHDL code for the 4-bit key-controlled arithmetic circuit.
- 2) observations and comments.