 

Digital System Design

Lecture 1

Design Concepts and Programmable Logic

Design Concepts



- **Reading Assignment:**

- Brown, “Fundamentals of Digital Logic with VHDL,
pp. 2 - 16, pp. 56 - 65

- **Learning Objective:**

- A general introduction to the process of designing digital systems
- Explain CAD tools

Chip Complexity

- **1963: transistor size = $50\mu\text{m}$**
- **1975: transistor size = $10\mu\text{m}$**
- **1985: transistor size = $2\mu\text{m}$**
- **1995: transistor size = $0.35\mu\text{m}$**
- **2004: transistor size = 90nm**
- **2012: transistor size = 36nm**
- **2018: transistor size = 10nm**

($1\mu\text{m} = 10^3 \text{ nm}$)




decreasing

SIA Roadmap


Table 1.1 A sample of the International Technology Roadmap for Semiconductors.

	Year					
	2006	2007	2008	2009	2010	2012
Technology feature size	78 nm	68 nm	59 nm	52 nm	45 nm	36 nm
Transistors per cm ²	283 M	357 M	449 M	566 M	714 M	1,133 M
Transistors per chip	2,430 M	3,061 M	3,857 M	4,859 M	6,122 M	9,718 M


A silicon wafer

 


The basic design loop

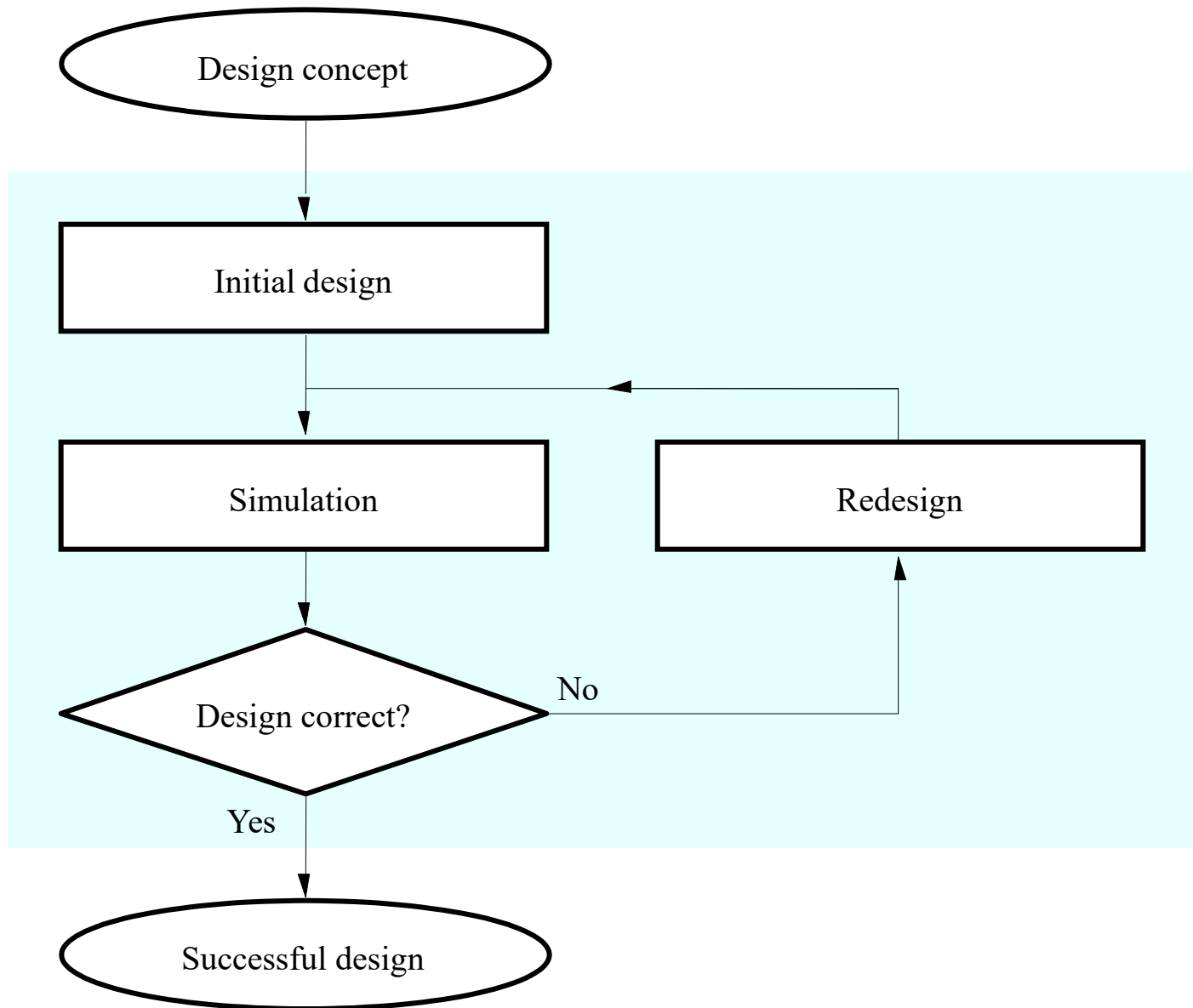


Levels of design abstraction

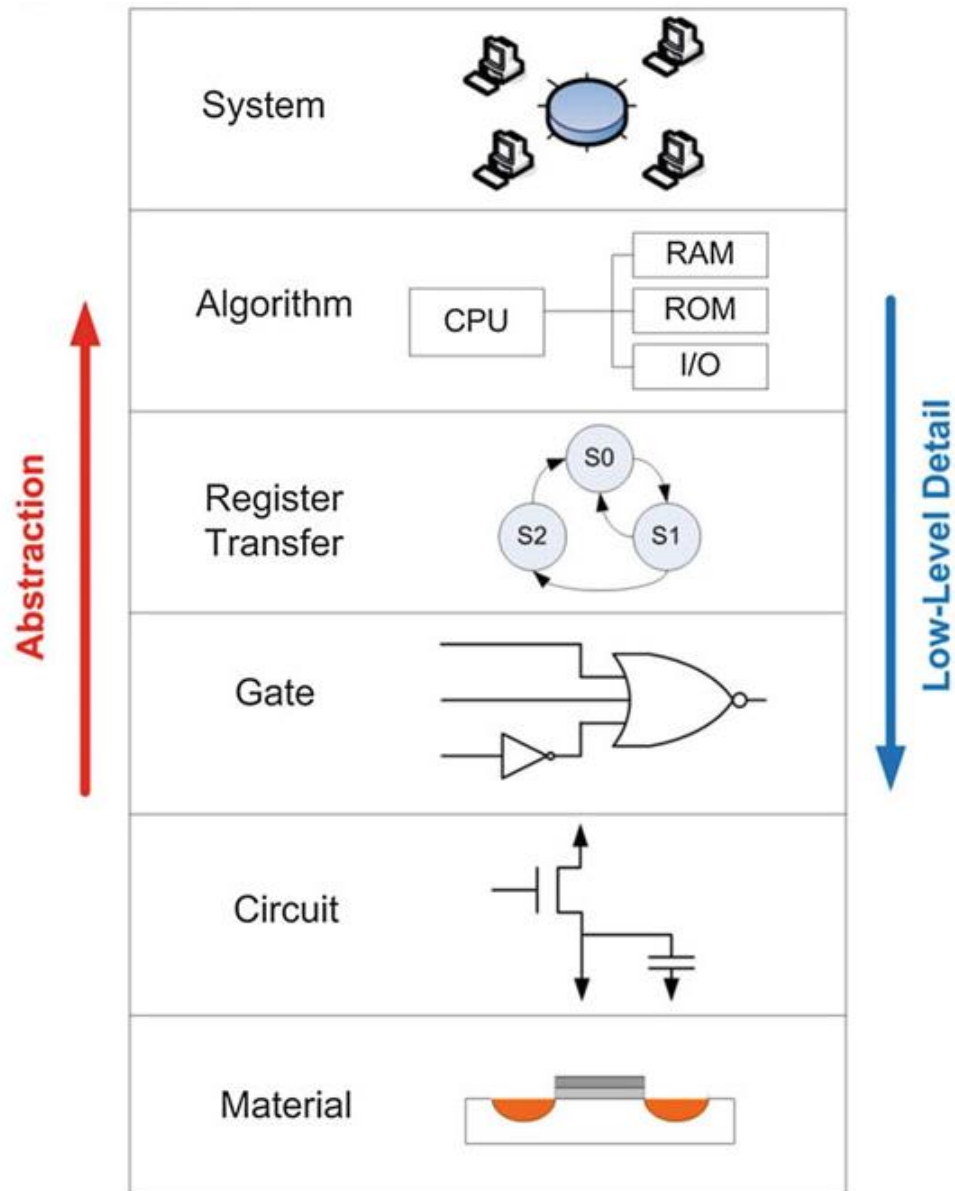


Generic design flow

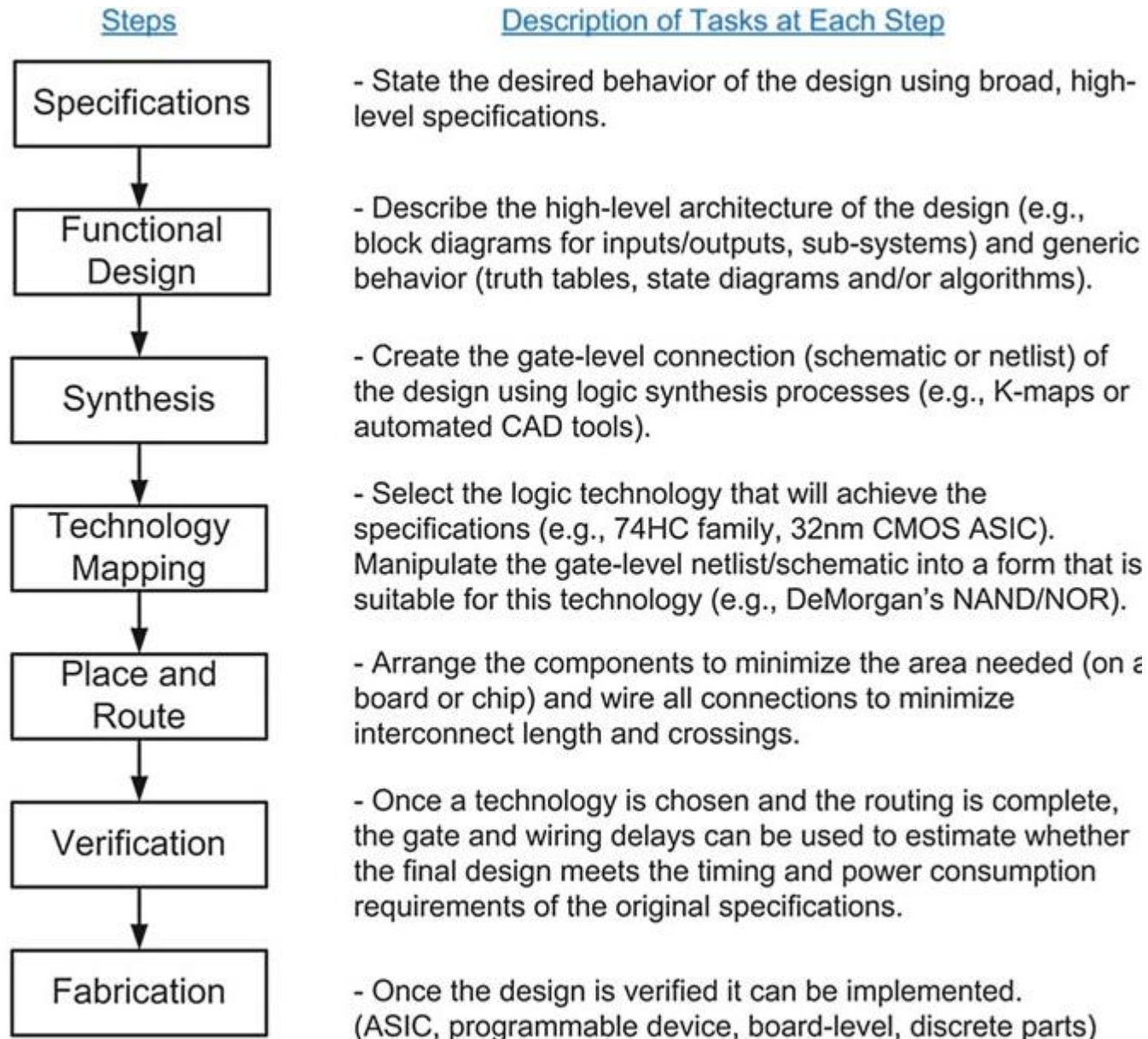

Classical design flow


 


 - Design a "Prime Number Detector" that takes in values from 0_{10} to 7_{10} . The circuit should be able to indicate a prime number with a delay less than 200ns.




A	B	C	PN
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

  
Red arrows point to the prime numbers: 2, 3, 5, and 7.



 
- It is decided that a 74HC logic family will be the most cost-effective technology for this design. To minimize the number of parts, the logic will be implemented with only NAND-gates.




Classical design flow

 

 - The circuit to be implemented is placed in a floor plan and an estimate of the connections are made.



 
- Based on the layout, the wire delays are found. The delays of the gates are taken from the data sheet.




- The verified circuit is implemented in hardware.



Modern design flow

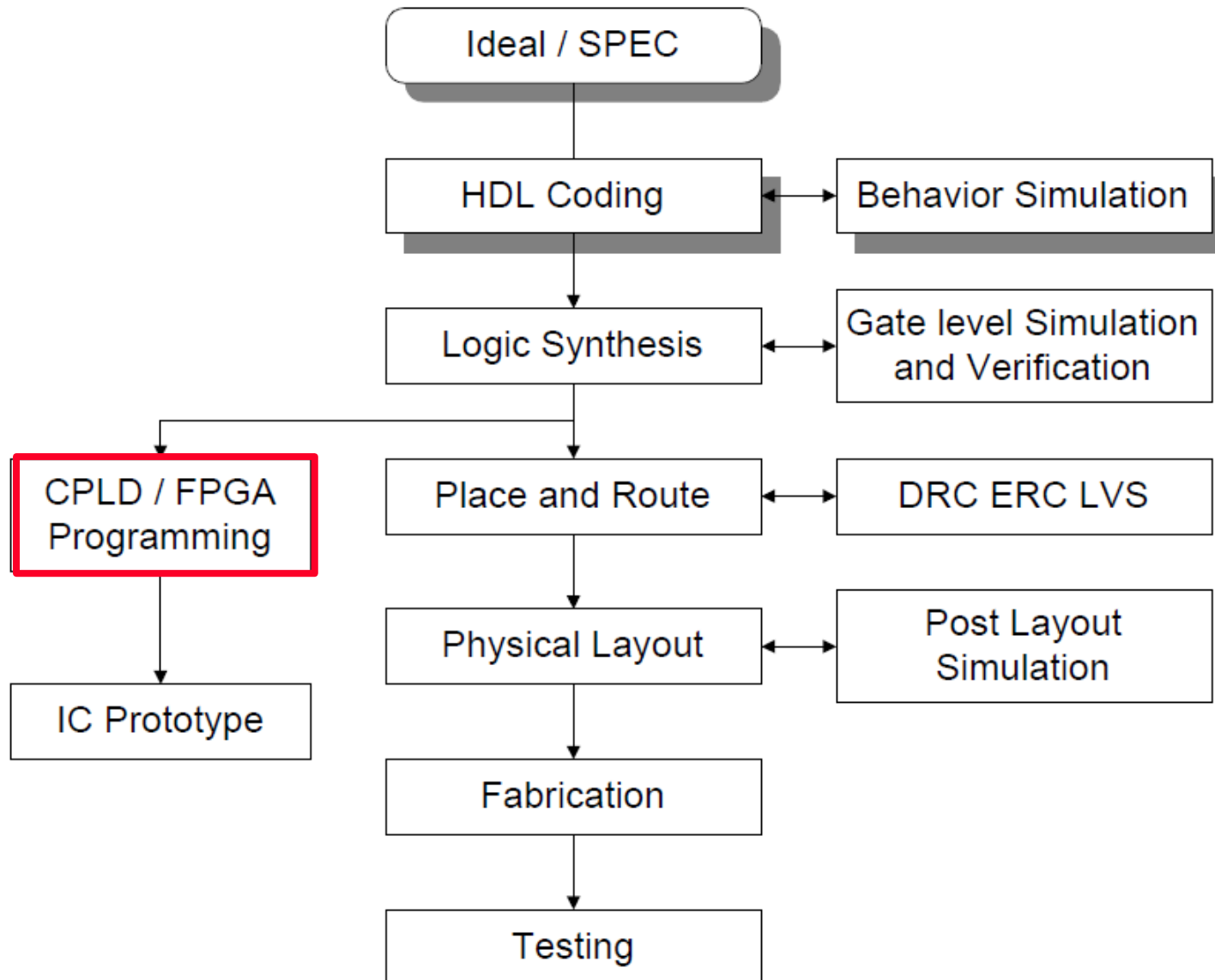



Altera DE0

 


Introduction to CAD tools

◦ Design Entry

  - Truth tables
 - Using Waveform Editor
- Schematic capture
 - Interconnect symbols in some *library*.
- Hardware description languages (HDLs).
 - Similar to a programming language.
 - VHDL and Verilog HDL.
 - Allow for sharing and design reuse.
 - Support hierarchical design.



Introduction to CAD tools (cont.)

 

```
ENTITY example1 IS
```

```
    PORT ( x1, x2, x3   : IN    BIT ;  
           f            : OUT  BIT ) ;
```

```
END example1 ;
```

```
ARCHITECTURE LogicFunc OF example1 IS
```

```
BEGIN
```

```
    f <= (x1 AND x2) OR (NOT x2 AND x3) ;
```

```
END LogicFunc ;
```

Introduction to CAD tools (cont.)

◦ **Logic synthesis or logic optimization**

- is process to translate a truth table, schematic, or VHDL code into a network of logic gates.

◦ **Simulation**

- **Functional simulation** is used to determine if designed circuit operates functionally correct.
 - Zero delay
- **Timing simulation** is used to check the performance of a design
 - Real delay

Programmable Logic



- **Reading Assignment:**

- Brown, “Fundamentals of Digital Logic with VHDL, pp. 98 - 114



- **Learning Objective:**

- Describe the genesis of programmable logic devices
- List the differences between complex programmable logic devices (CPLDs) and field programmable gate arrays (FPGAs) and describe the basic organization of each


Overview

- The first programmable logic devices (**PLDs**) were programmable logic arrays (**PLAs**)
- **PLAs** are combinational, **two-level AND-OR** devices that can be programmed to realize sum-of-products expression
- General structure of a PLA

$PLA \subseteq PLD$

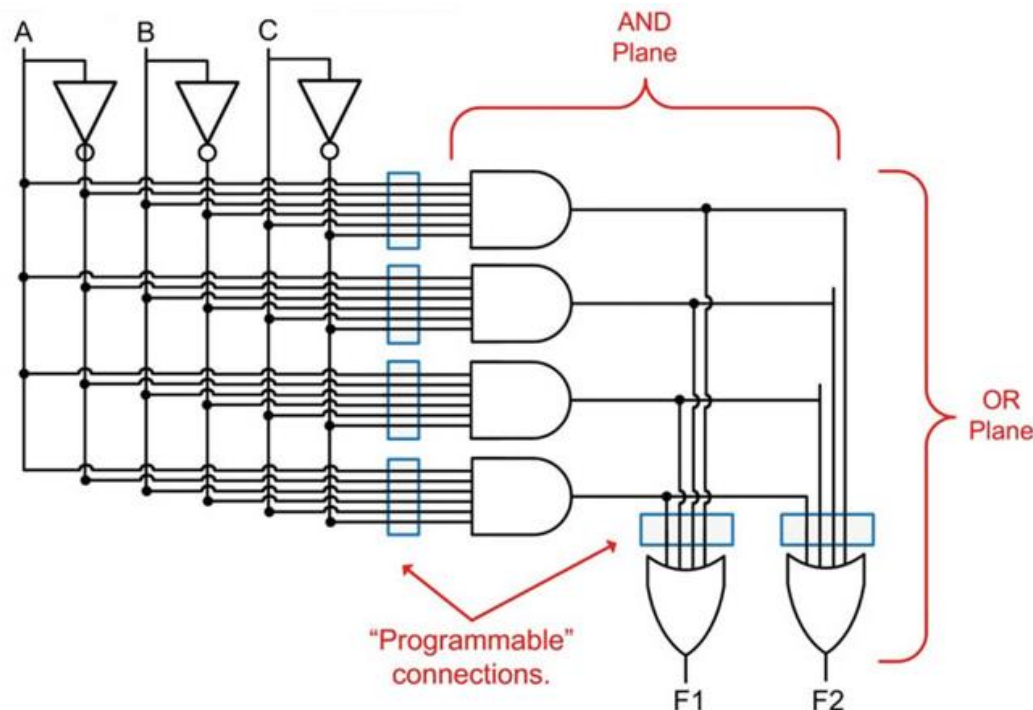 


 Simplified Programmable Logic Array (PLA)




Constants

 - Sometimes a PLA output must be programmed to be a constant 1 or a constant 0.
 - P1 is always 1 because its product line is connected to no inputs and is therefore always pulled HIGH;
 - this constant-1 term drives the O1 output.
- No product term drives the O2 output, which is therefore always 0.
- Another method of obtaining a constant-0 output is shown for O3.




Programmable Array Logic (PAL)

 
- A special case of PLA is the programmable array logic (PAL)
- Unlike a PLA, a PAL device has a fixed OR array (i.e. AND gates can not be shared)



AND plane

An example of a PAL

 


 

• PAL v.s. PLA


Macrocell (一組)

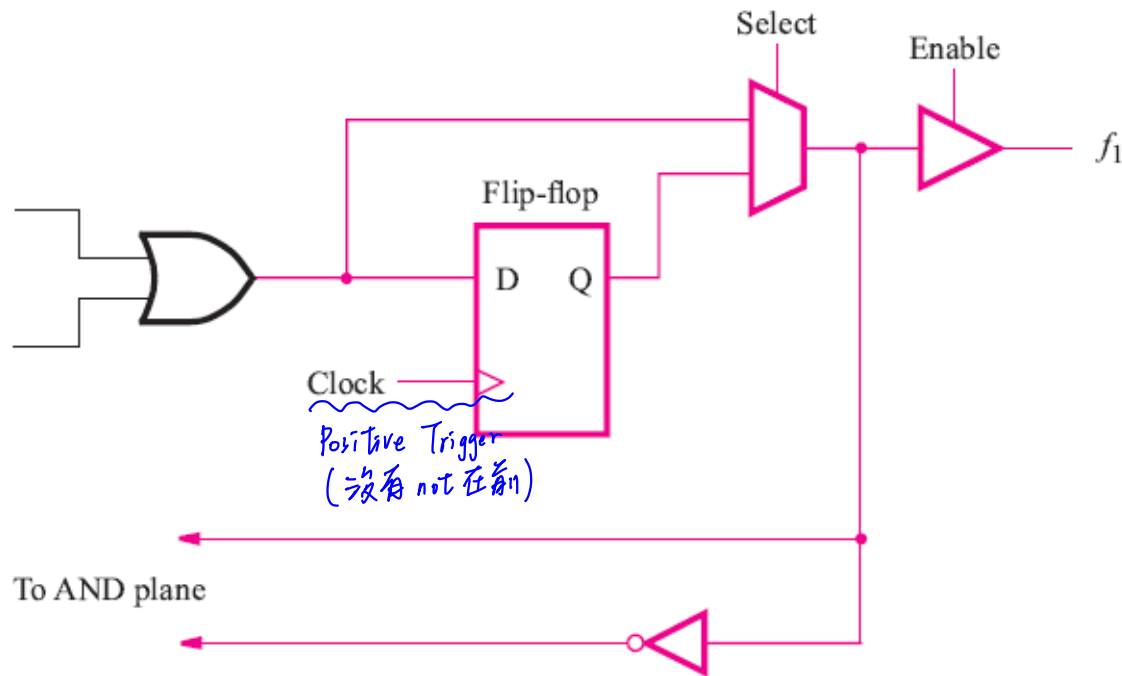- In many PALs, extra circuitry is added at the output of each OR gate to provide additional flexibility.
- It is customary to use the term **macrocell** to refer to the OR gate combined with the extra circuitry.




Complex PLDs (CPLDs)

- PLAs and PALs are limited to fairly modest sizes, typically supporting a combined number of inputs plus outputs of not more than 32.
- For implementation of circuits that require **more inputs and outputs**, a more sophisticated type of chip, called a **complex programmable logic device (CPLD)**, can be used
- A CPLD comprises multiple PAL-like circuit blocks on a single chip, with internal wiring resources to connect the circuit blocks.

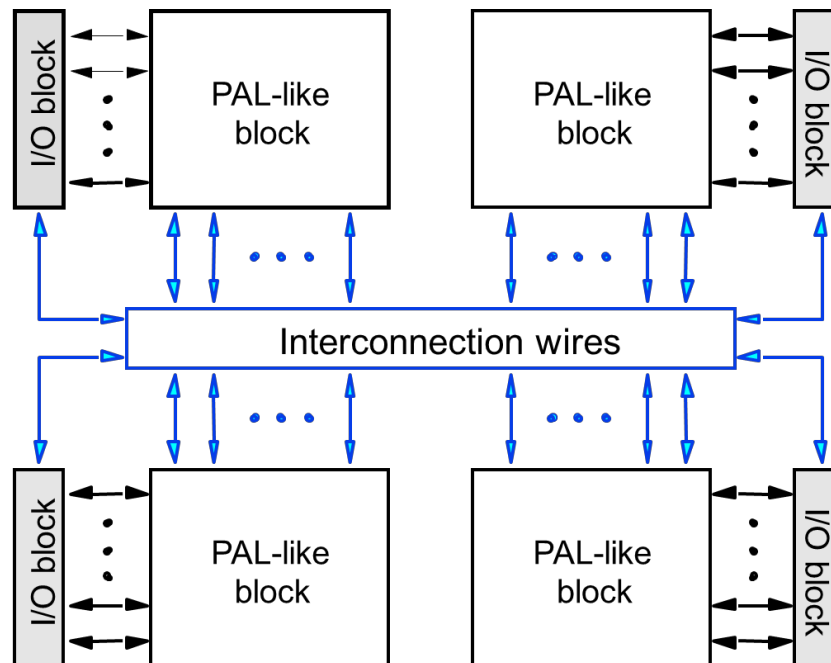


A section of a CPLD (3 macrocell)

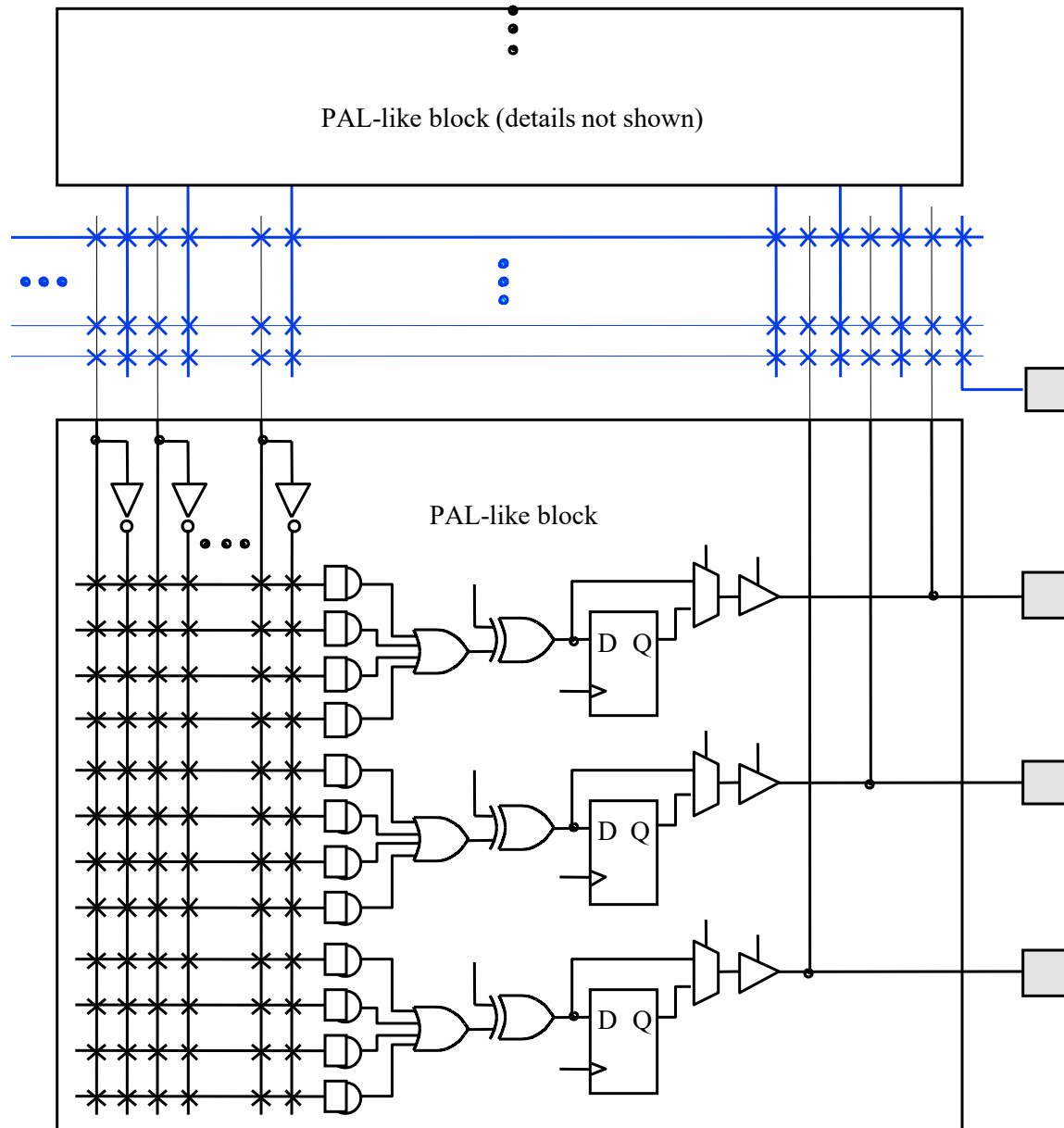

Field Programmable Gate Array (FPGA)



- By modern standards, a logic circuit with 10,000 gates is not large. To implement larger circuits, it is convenient to use a different type of chip that has a larger logic capacity.
- **Field-programmable gate array (FPGA)** is a programmable logic device that supports implementation of relatively large logic circuits.
- FPGAs provide **logic blocks** for implementation of the required functions.

 

Field Programmable Gate Array (FPGA)

- Each logic block in an FPGA typically has a small number of inputs and outputs.
- The most commonly used logic block is a lookup table (LUT), which contains storage cells that are used to implement a small logic function.
- Each cell is capable of holding a single logic value, either 0 or 1.
- LUTs of various sizes may be created, where the size is defined by the number of inputs.

2 variable's LUT

  


0	0	0	0
0	0	1	1
0	1	0	0
1	1	1	1


可知為 $(A \oplus B \oplus C)$
if odd 1's output 1
otherwise $\rightarrow 0$

Using MUX implement AND gate

• 4-1 MUX

 

• 2-1 MUX

 


Field Programmable Gate Array (FPGA)

- A two-input lookup table (LUT).


x_1	x_2	f_1
0	0	1
0	1	0
1	0	0
1	1	1

(b) $f_1 = \bar{x}_1\bar{x}_2 + x_1x_2$

 


(c) Storage cell contents in the LUT

- Inclusion of a flip-flop with a LUT

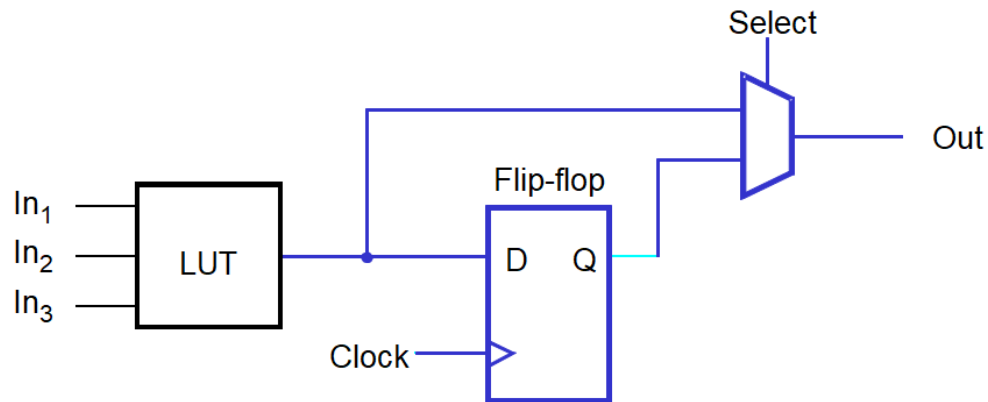

A section of a programmed FPGA



$$f = f_1 + f_2 = x_1x_2 + x_2'x_3$$

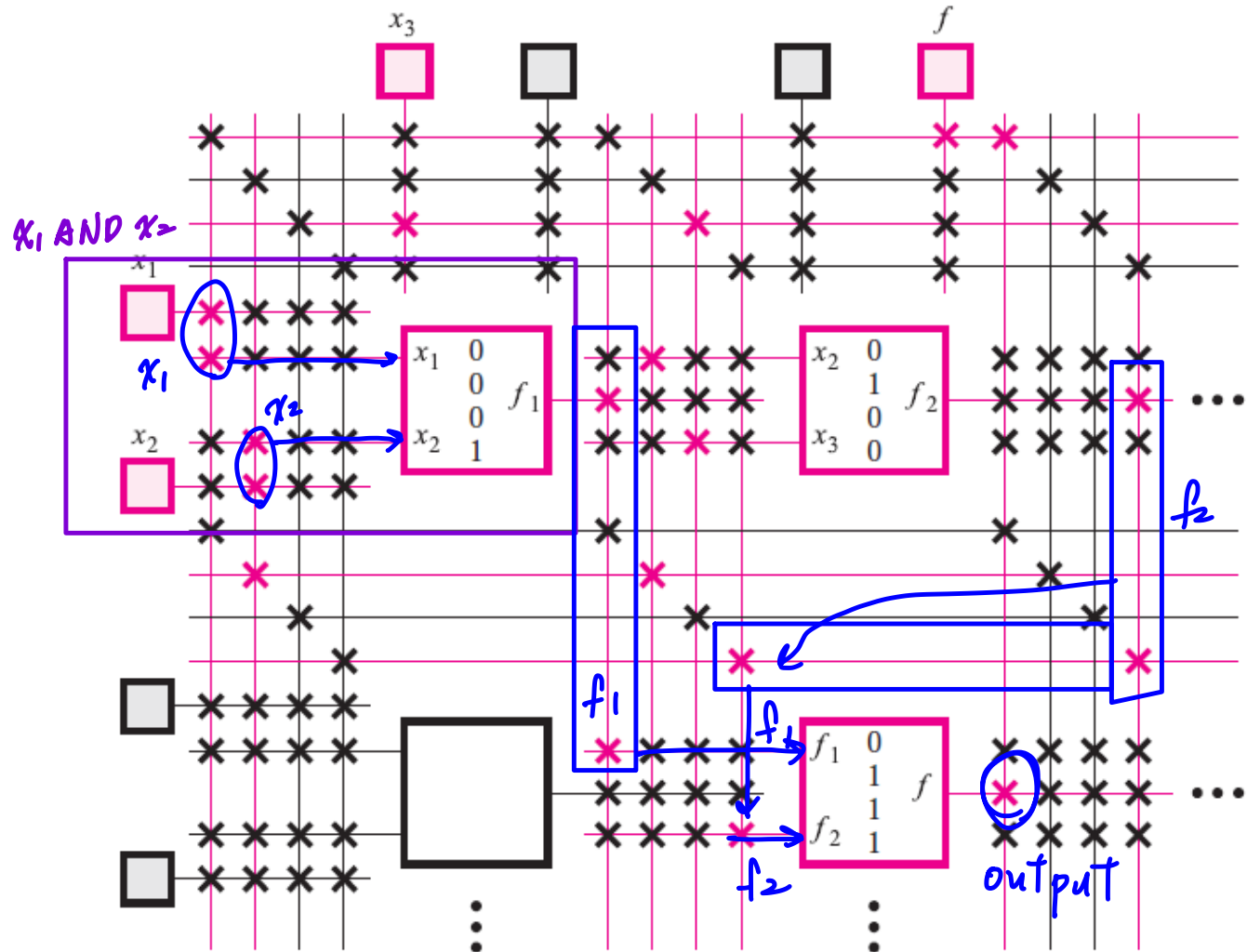


FPGA Programmable Interconnect

A simple model for a programmable interconnection is an NMOS transistor that connects or disconnects two wires. The switch is controlled using a configuration bit.

  
This can be used in a variety of configurations.



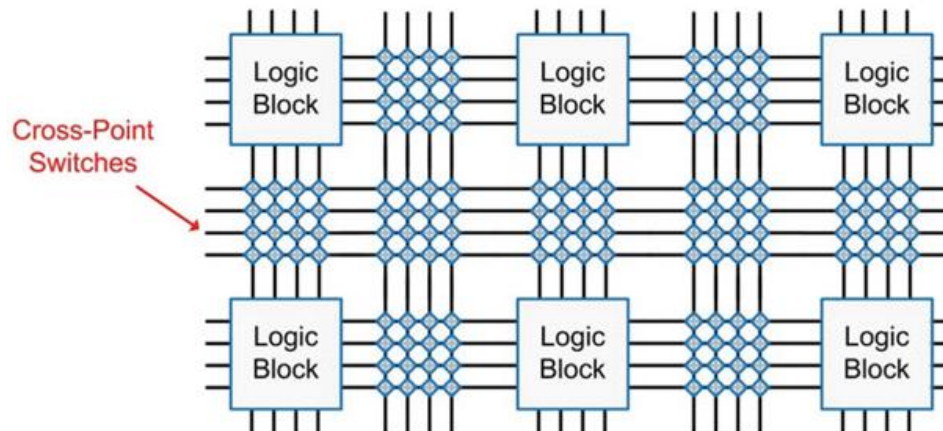The switches are placed at the intersections of horizontal and vertical routing lanes on the FPGA.



FPGA I/O Blocks

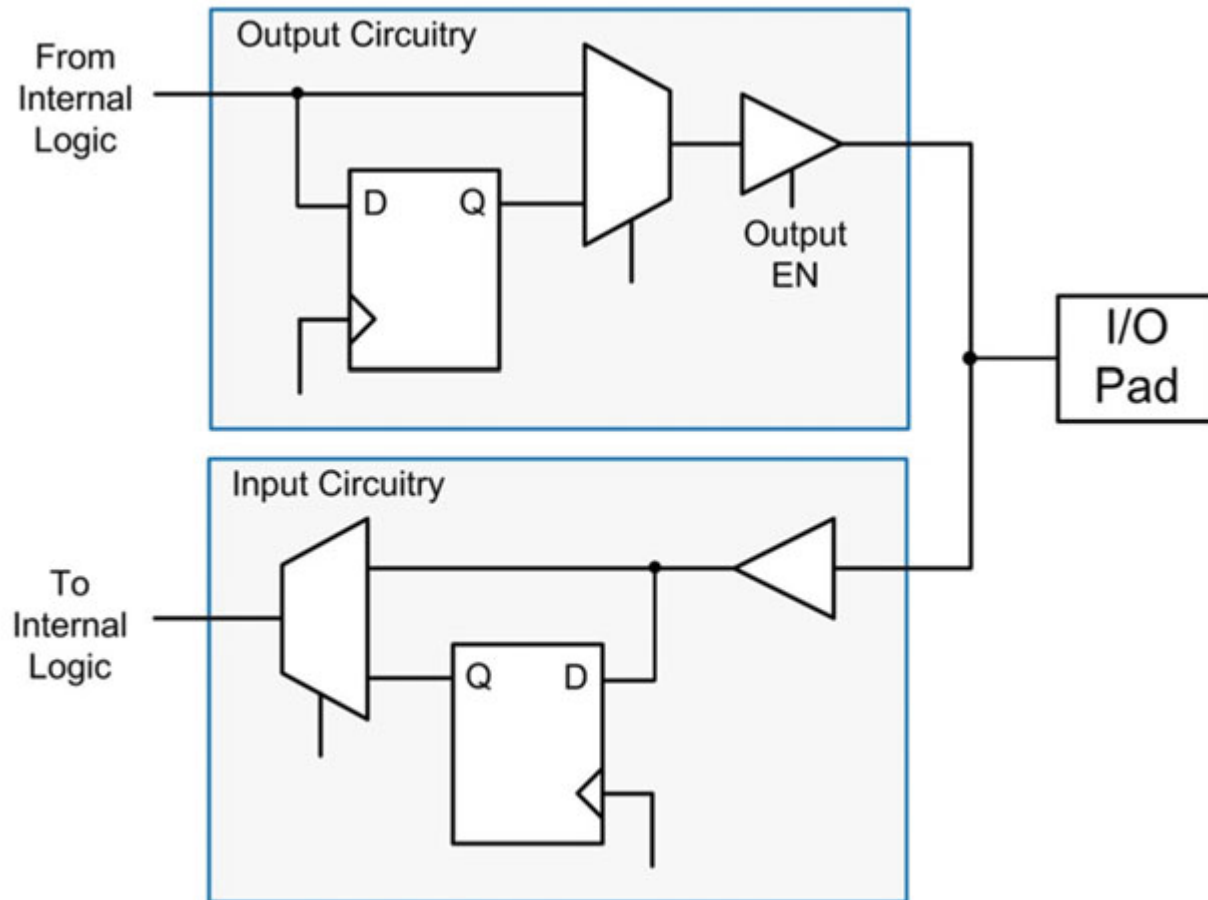

Summary

- There are currently two types of programmable logic devices in common use:
 - **CPLDs**
 - in-circuit programmable
 - non-volatile (retains configuration information when powered down)
 - “instant on” (no external configuration ROM or boot sequence required)
 - less dense (fewer programmable logic blocks) than comparably sized FPGA
 - **FPGAs**
 - in-circuit programmable
 - volatile (loses configuration when powered down)
 - requires external configuration ROM and “boot” sequence to initialize
 - more dense (greater number programmable logic blocks) than comparably sized CPLD